

Digital Design & Computer Arch.

Lecture 5: Hardware Description Languages and Verilog

Prof. Onur Mutlu

ETH Zürich

Spring 2026

5 March 2026

We Covered Combinational Logic (I)

- Building blocks of modern computers
 - Transistors
 - Logic gates
- Combinational logic circuits
- Boolean algebra
- Using Boolean algebra to represent combinational circuits
- Basic combinational logic blocks
- Simplifying combinational logic circuits

We Covered Combinational Logic (II)

- Basic logic gates (AND, OR, NOT, NAND, NOR, XOR)
 - Decoder
 - Multiplexer
 - Full Adder
 - Programmable Logic Array (PLA)
 - Comparator
 - Arithmetic Logic Unit (ALU)
 - Tri-State Buffer
-
- Standard form representations: SOP & POS
 - Logic simplification via Boolean Algebra
 - Logical completeness

We Covered Sequential Logic

■ Circuits that can store information

- ❑ Cross-coupled inverter
- ❑ R-S Latch
- ❑ Gated D Latch
- ❑ D Flip-Flop
- ❑ Register
- ❑ Memory

■ Sequential logic circuits

- ❑ State & Clock
- ❑ Asynchronous vs. Synchronous

■ Finite State Machines (FSM)

- ❑ How to design FSMs

Agenda for Today

- Hardware Description Languages
- Implementing Combinational Logic (in Verilog)
- Implementing Sequential Logic (in Verilog)
- The Verilog slides constitute a tutorial. We may not cover all.
- All slides will be beneficial for your labs

What We Will Cover Soon: LC-3 Processor

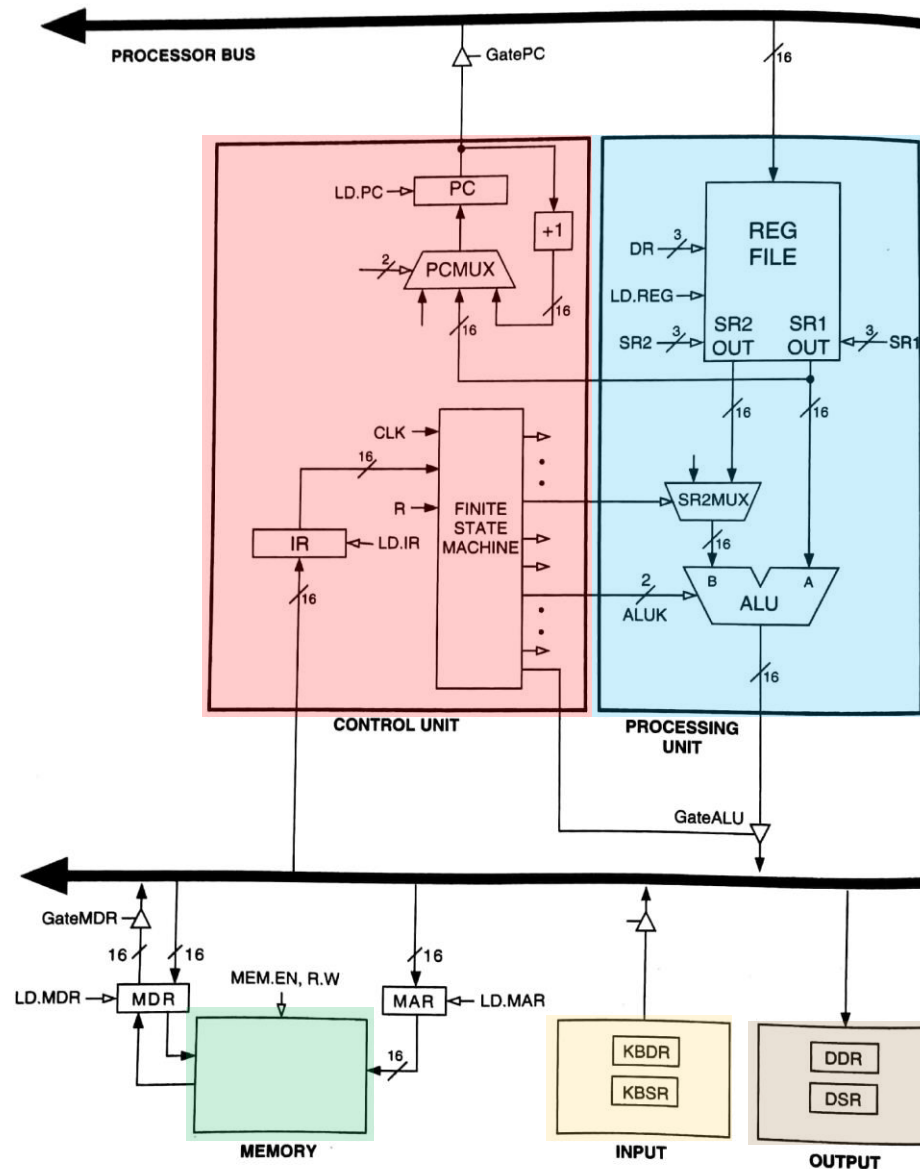


Figure 4.3 The LC-3 as an example of the von Neumann model

The diagram illustrates the MARMAC architecture, a complex digital logic system. Key components and their interconnections include:

- Control and State Elements:**
 - PC (Program Counter):** Receives **LD.PC** and **GatePC** signals. Its output goes to **PCMUX** and **ADDR1MUX**.
 - PCMUX (Program Counter Multiplexer):** Selects between **PC** and **PC+1** (via a **+1** incrementer).
 - REG FILE (Register File):** Receives **LD.REG** and **DR** (3-bit) signals. It outputs **SR1 OUT** (3-bit) and **SR2 OUT** (3-bit).
 - SR2MUX (Status Register 2 Multiplexer):** Selects between **SR2 OUT** and **PC** based on a control signal.
 - ALU (Arithmetic Logic Unit):** Receives **SR2MUX** output and **PC** output. It performs operations based on **ALUK** (2-bit) and **GateALU** signals. Its output goes to **OUTPUT**.
 - FINITE STATE MACHINE:** Receives **R** (3-bit) and **LD.CC** signals. It outputs **NZP** (3-bit) and **LOGIC** signals.
 - LOGIC:** Receives **LD.CC** and **LOGIC** signals. It outputs **NZP**.
- Data Path and Addressing:**
 - ADDR1MUX (Address 1 Multiplexer):** Selects between **PC** and **PC+1** based on **GatePC**.
 - ADDR2MUX (Address 2 Multiplexer):** Selects between **PC** and **PC+1** based on **GatePC**.
 - SEXT (Sign Extension):** Multiple **SEXT** blocks are used to extend the sign of data from 7-bit, 10-bit, 8-bit, and 5-bit sources to 16-bit.
 - IR (Instruction Register):** Receives **LD.IR** and **GateMARMUX** signals. It outputs **SEXT** signals.
 - MARMUX (Memory Address Multiplexer):** Selects between **PC** and **PC+1** based on **GateMARMUX**.
 - PC+1:** A 16-bit incrementer that takes **PC** output and adds 1.
- Memory and I/O:**
 - MEMORY:** Receives **MEM.EN. R.W** (Memory Enable/Read/Write) and **LD.MDR** signals. It outputs **LD.MDR** and **LD.MAR** signals.
 - MAR (Memory Address Register):** Receives **LD.MAR** and **GateMARMUX** signals. It outputs **LD.MAR** and **LD.MDR** signals.
 - INPUT:** Receives **LD.MDR** and **GateMARMUX** signals. It outputs **LD.MDR** and **LD.MAR** signals.
 - OUTPUT:** Receives **LD.MDR** and **GateMARMUX** signals. It outputs **LD.MDR** and **LD.MAR** signals.

Readings (This Week)


- Hardware Description Languages and Verilog
 - H&H Chapter 4 in full
- Timing and Verification
 - H&H Chapters 2.9 and 3.5 + (start Chapter 5)

Who Painted This Painting?



Salvador Dali @ 1924

What About This?

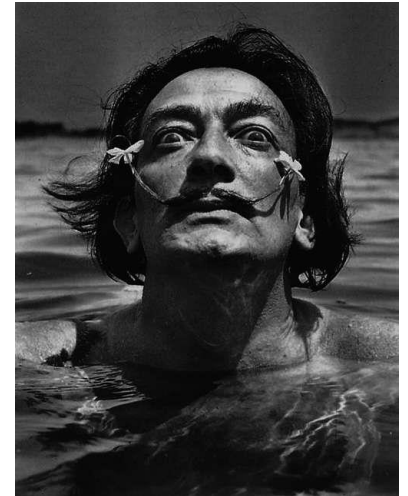

Salvador Dali @ 1937

Takeaway

Learn the basic principles


before you can

consciously choose to

use, ignore (or even break) them

Hardware Description Languages & Verilog


2017: Intel Kaby Lake

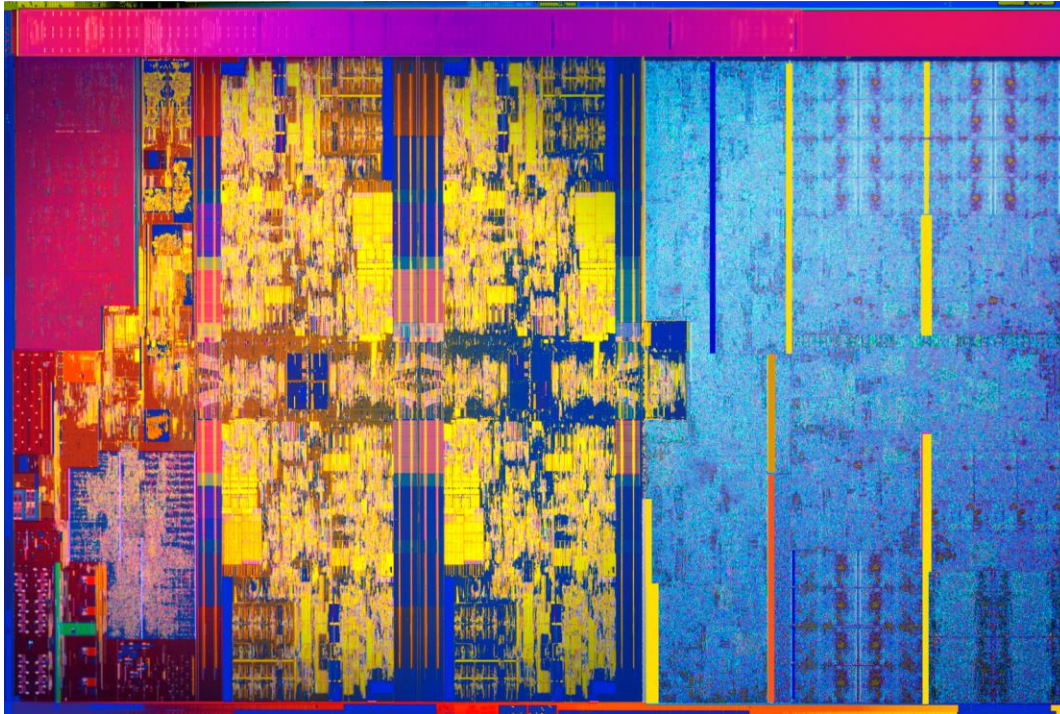

https://en.wikichip.org/wiki/intel/microarchitectures/kaby_lake


- 64-bit processor
- 4 cores, 8 threads
- 14-19 stage pipeline
- 3.9 GHz clock freq.
- **1.75B transistors**
- In ~47 years, about 1,000,000-fold growth in transistor count and performance!

2021: Apple M1

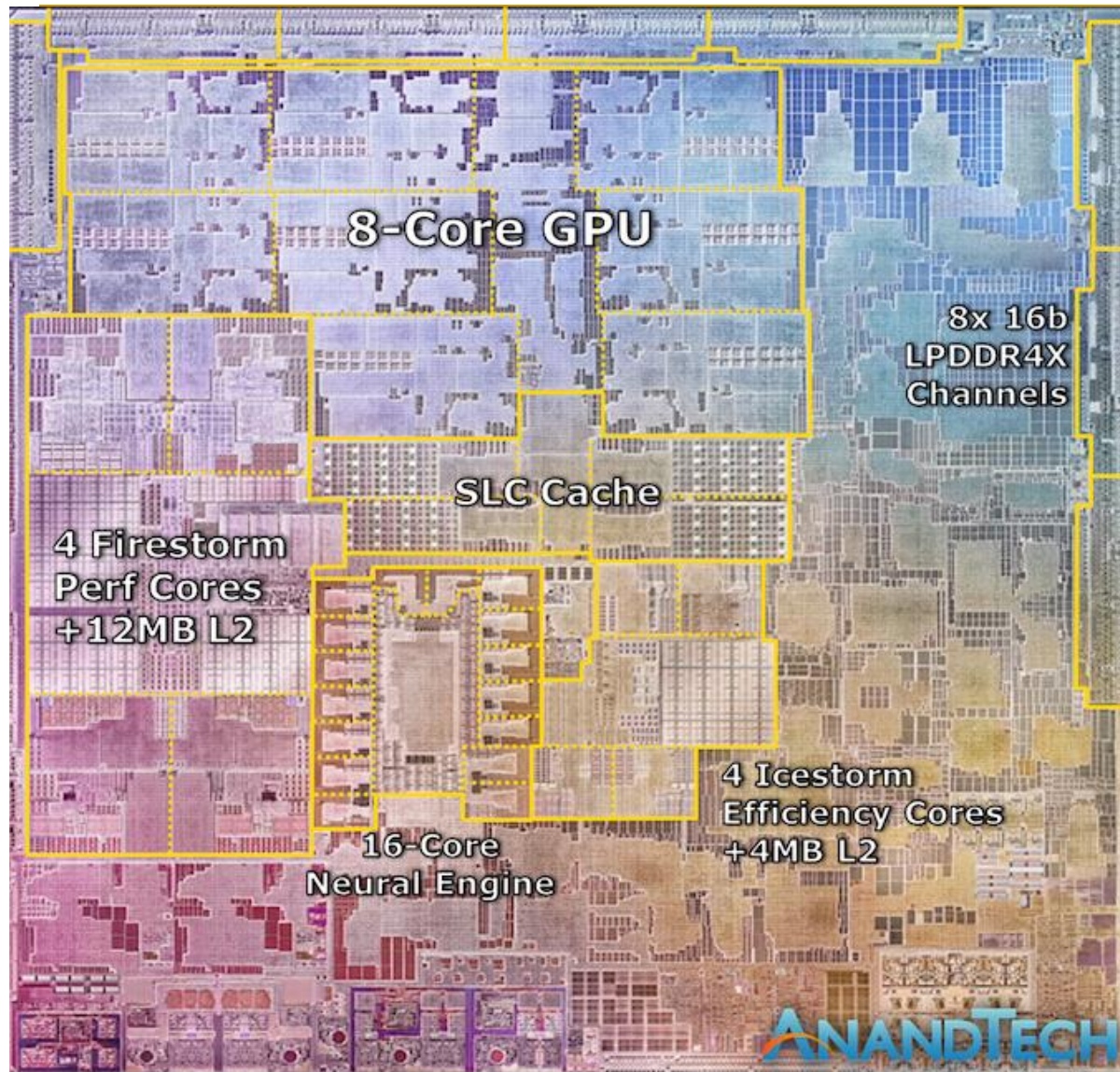


- 4 High-Perf GP Cores
- 4 Efficient GP Cores
- 8-Core GPU
- 16-Core Neural Engine
- Lots of Cache
- Many Caches
- 8x Memory Channels
- 16B transistors

2022: Apple M1 Ultra

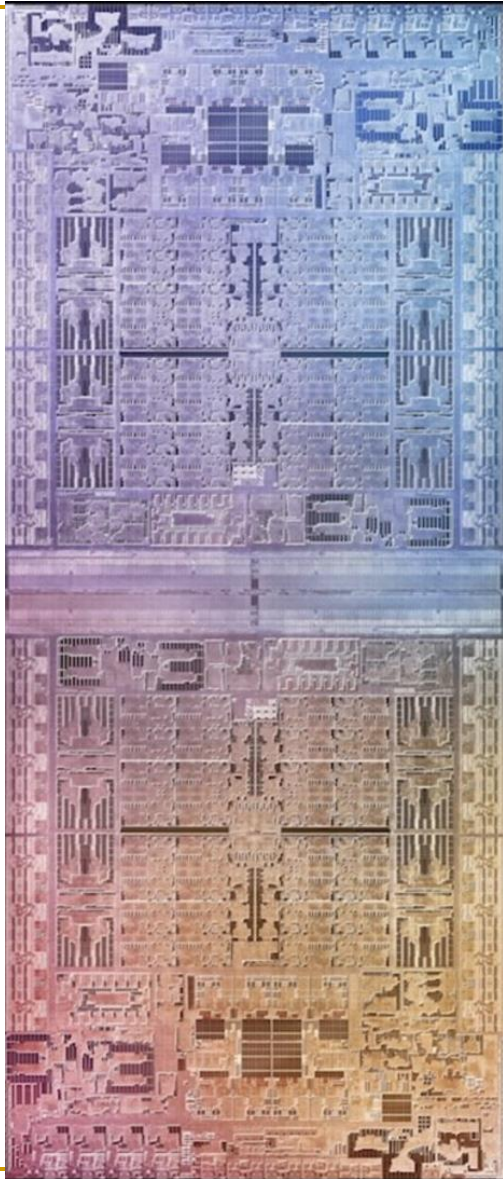

- 16 High-Perf GP Cores
- 4 Efficient GP Cores
- 64-Core GPU
- 32-Core Neural Engine
- Lots of Cache
- Many Caches
- 32x Memory Channels
- 128 GB DRAM
- 114B transistors

2019: Cerebras Wafer Scale Engine

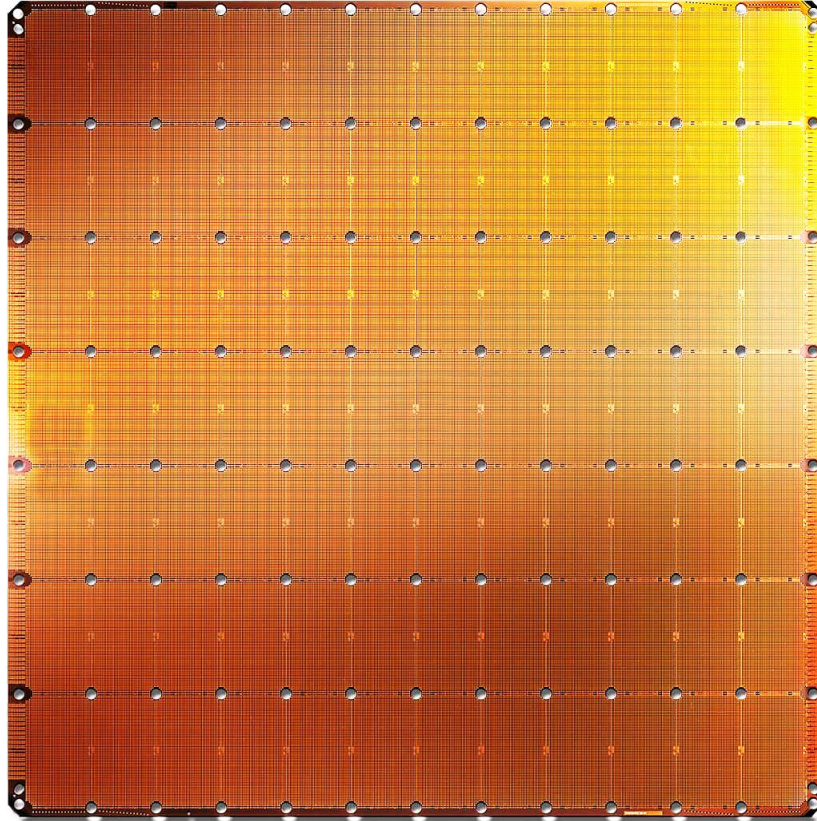

Cerebras WSE
1.2 Trillion transistors
46,225 mm²

- The largest ML accelerator chip (2019)
- 400,000 cores




Largest GPU
21.1 Billion transistors
815 mm²

NVIDIA TITAN V

<https://www.anandtech.com/show/14758/hot-chips-31-live-blogs-cerebras-wafer-scale-deep-learning>

<https://www.cerebras.net/cerebras-wafer-scale-engine-why-we-need-big-chips-for-deep-learning/> 16

2021: Cerebras Wafer Scale Engine 2

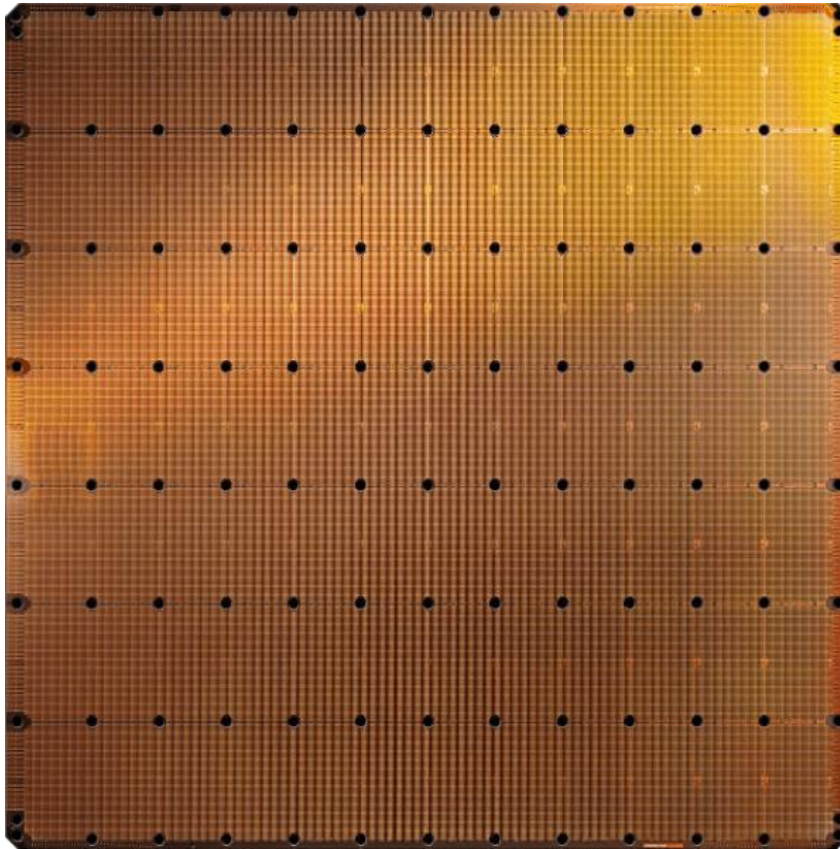

Cerebras WSE-2
2.6 Trillion transistors
46,225 mm²

- The largest ML accelerator chip (2021)
- 850,000 cores




Largest GPU
54.2 Billion transistors
826 mm²

NVIDIA Ampere GA100

<https://www.anandtech.com/show/14758/hot-chips-31-live-blogs-cerebras-wafer-scale-deep-learning>

<https://www.cerebras.net/cerebras-wafer-scale-engine-why-we-need-big-chips-for-deep-learning/>

2023: Cerebras's Wafer Scale Engine 3

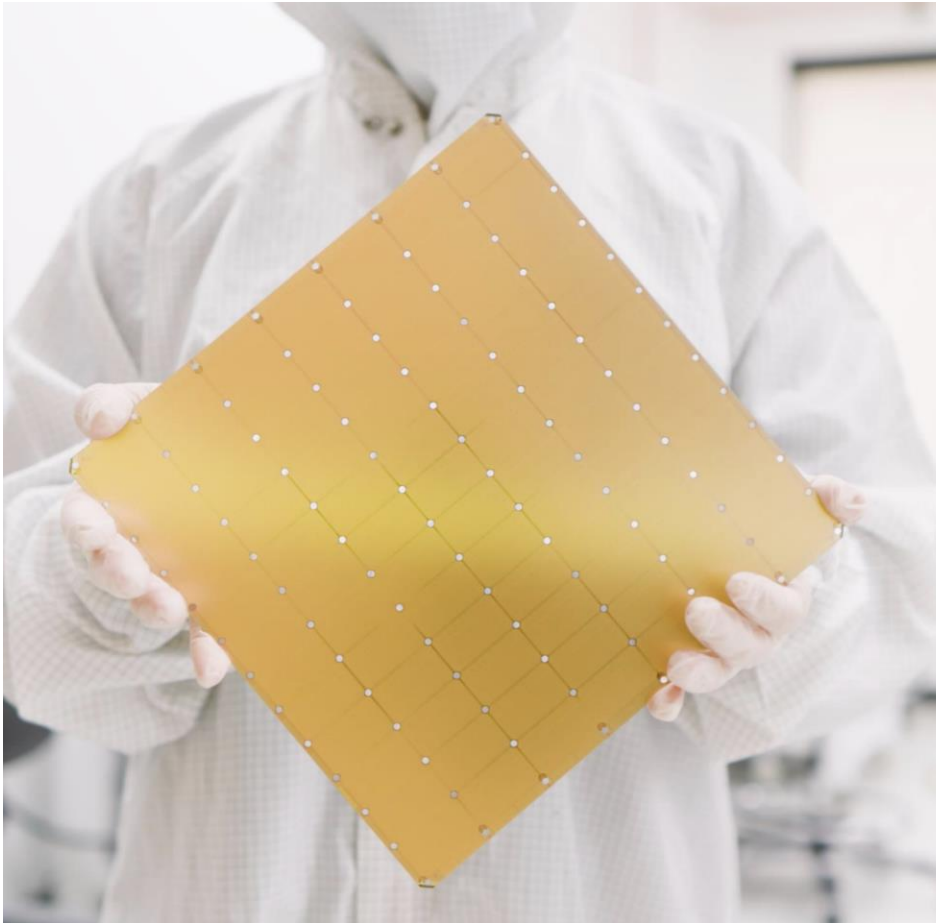

Cerebras Wafer-Scale Engine

The largest chip ever produced

46,225 mm² silicon

4 trillion transistors

900,000 AI cores

125 Petaflops of AI compute

44 Gigabytes of on-chip memory

21 PByte/s memory bandwidth

214 Pbit/s fabric bandwidth

5nm TSMC process

Transistor Counts Are Growing

Year	Component	Name	Number of MOSFETs (in trillions)	Remarks
2022	Flash memory	Micron's V-NAND module	5.3	stacked package of sixteen 232-layer 3D NAND dies
2020	any processor	Wafer Scale Engine 2	2.6	wafer-scale design of 84 exposed fields (dies)
2024	GPU	Nvidia B100	0.208	Uses two reticle limit dies, with 104 billion transistors each, joined and acting as a single large monolithic piece of silicon
2025	Microprocessor (consumer)	Apple M3 Ultra	0.184	SoC using two dies joined with a high-speed bridge

In terms of computer systems that consist of numerous integrated circuits, the [supercomputer](#) with the highest transistor count as of 2016 was the Chinese-designed [Sunway TaihuLight](#), which has for all CPUs/nodes combined "about 400 trillion transistors in the processing part of the hardware" and "the [DRAM](#) includes about 12 [quadrillion](#) transistors, and that's about 97 percent of all the transistors."^[6] To compare, the [smallest computer](#), as of 2018 dwarfed by a grain of rice, had on the order of 100,000 transistors.

Memory chips have orders of magnitude more transistors than computation chips

How to Deal with This Complexity?

- Hardware Description Languages
- What we need for hardware design:
 - Ability to describe (specify) complex designs
 - ... and to simulate their behavior (functional & timing)
 - ... and to synthesize (automatically design) portions of it
 - have an error-free path to implementation
- Hardware Description Languages enable all of the above
 - Languages designed to describe hardware
 - There are similarly-featured HDLs (e.g., **Verilog**, VHDL, ...)
 - if you learn one, it is not hard to learn another
 - mapping between languages is typically mechanical, especially for the commonly used subset

Hardware Description Languages

- **Two well-known hardware description languages**
- **Verilog**
 - ❑ Developed in 1984 by Gateway Design Automation
 - ❑ Became an IEEE standard (1364) in 1995
 - ❑ More popular in US
- **VHDL (VHSIC Hardware Description Language)**
 - ❑ Developed in 1981 by the US Department of Defense
 - ❑ Became an IEEE standard (1076) in 1987
 - ❑ More popular in Europe
- We will use Verilog in this course

Why Specialized Languages for Hardware?

- HDLs enable easy description of hardware structures
 - Wires, gates, registers, flip-flops, clock, rising/falling edge, ...
 - Combinational and sequential logic elements
- HDLs enable seamless expression of parallelism inherent in hardware
 - All hardware logic operates concurrently
- Both of the above ease **specification, simulation & synthesis**

Hardware Design Using HDL

Key Design Principle: Hierarchical Design

■ Design a hierarchy of modules

- ❑ Predefined “primitive” gates (AND, OR, ...)
- ❑ Simple modules are built by instantiating these gates (e.g., components like MUXes)
- ❑ Complex modules are built by instantiating simple modules, ...


■ Hierarchy controls complexity

- ❑ Analogous to the use of function/method abstraction in programming

■ Complexity is a BIG deal


- ❑ In real world, how big is the size of a module (that is described in HDL and then synthesized to gates)?
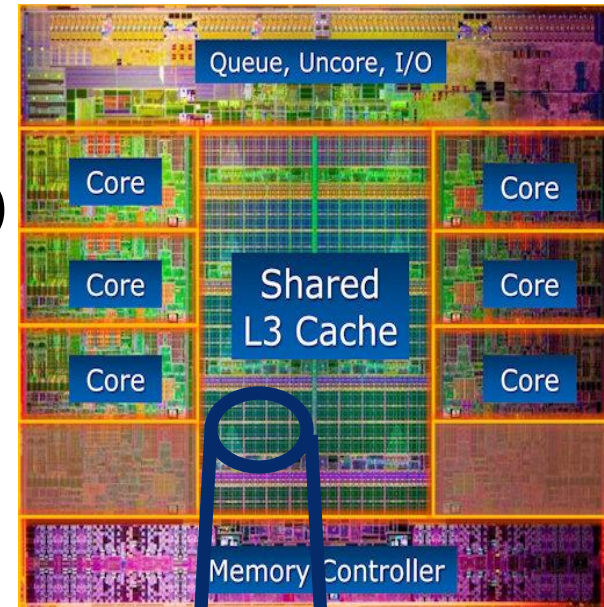
<https://techreport.com/review/21987/intel-core-i7-3960x-processor>




Top-Down Design Methodology

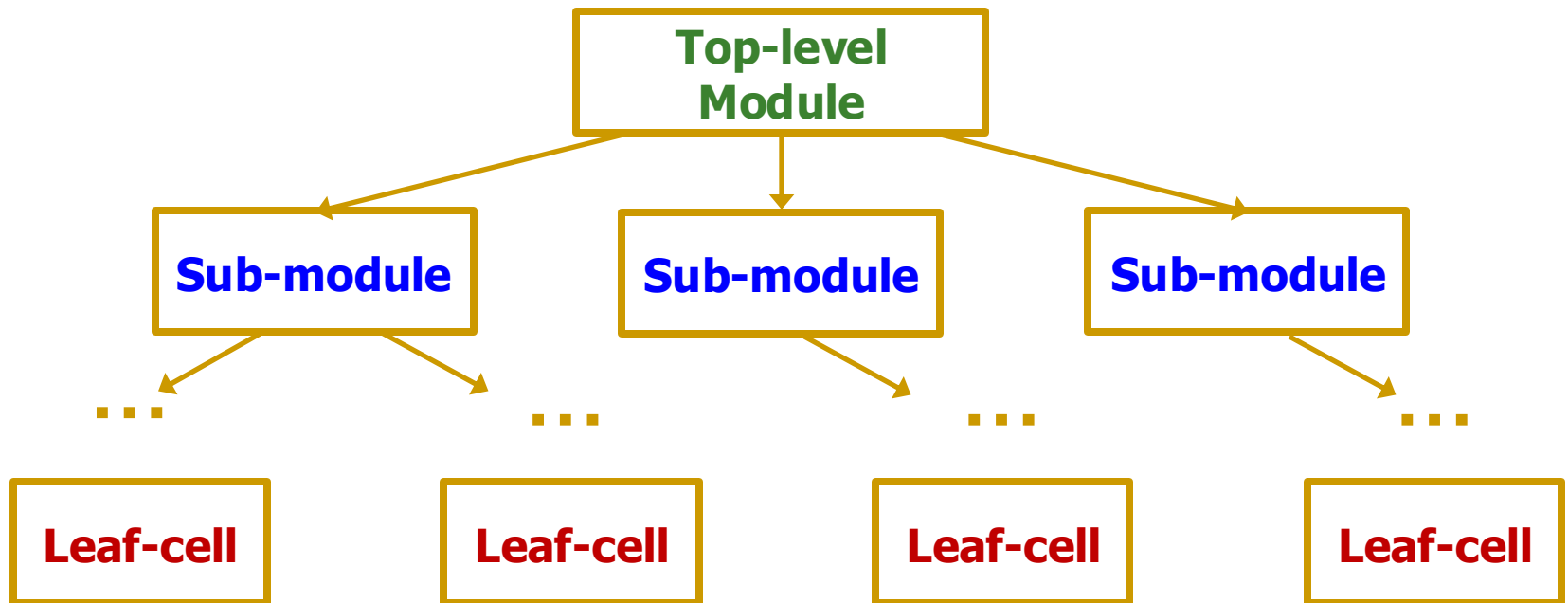- We define the **top-level module** and identify the **sub-modules** necessary to build the top-level module
- Subdivide the sub-modules until we come to **leaf cells**
 - **Leaf cell**: circuit components that cannot further be divided (e.g., *logic gates, primitive cell library elements*)




Bottom-Up Design Methodology

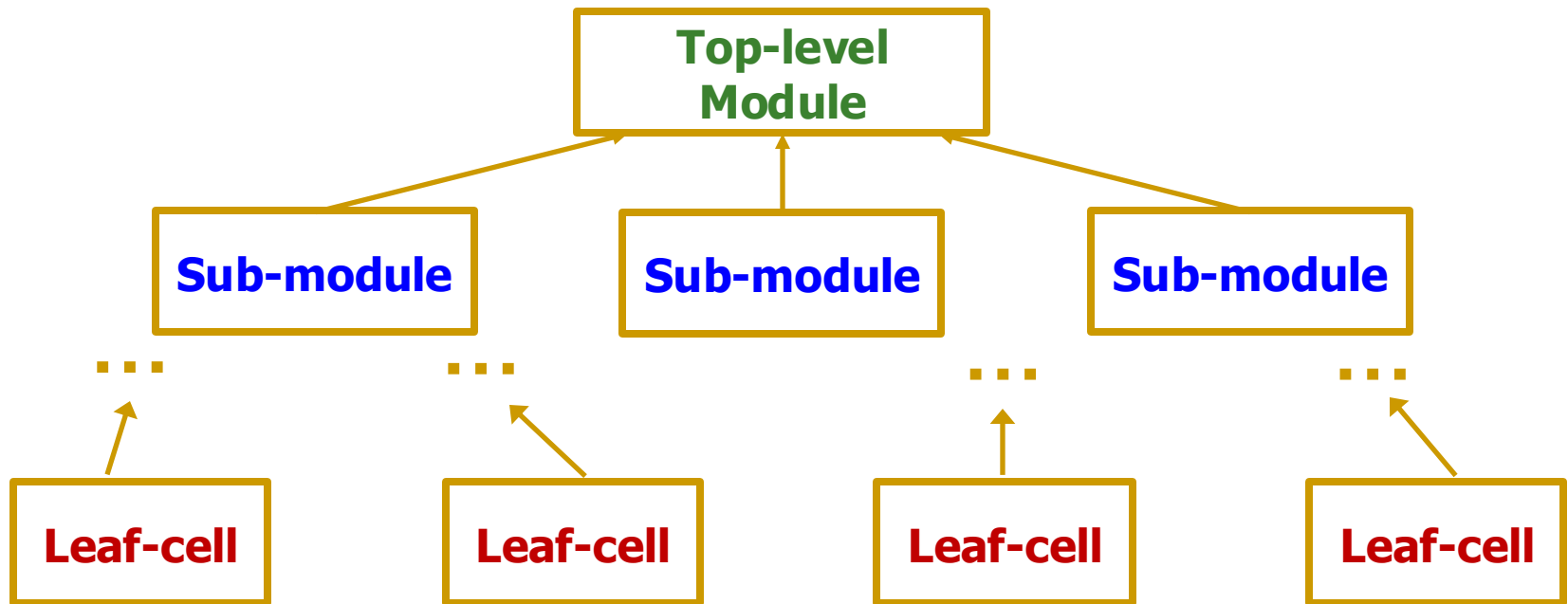- We first identify the **building blocks** that are available to us
- **Build bigger modules**, using these building blocks
- These modules are then used for higher-level modules until we build the **top-level module** in the design





Defining a Module in Verilog

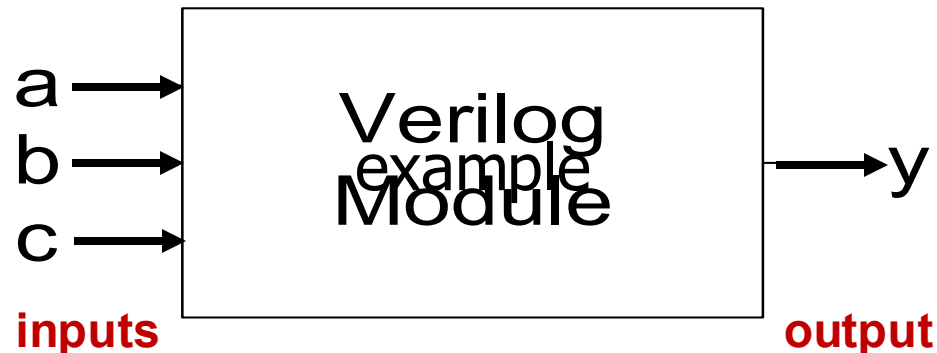- A **module** is the main building block in Verilog
- We first need to define:
 - **Name** of the module
 - **Directions** of its **ports** (e.g., **input**, **output**)
 - **Names** of its **ports**
- Then:
 - Describe the **functionality** of the module



Implementing a Module in Verilog

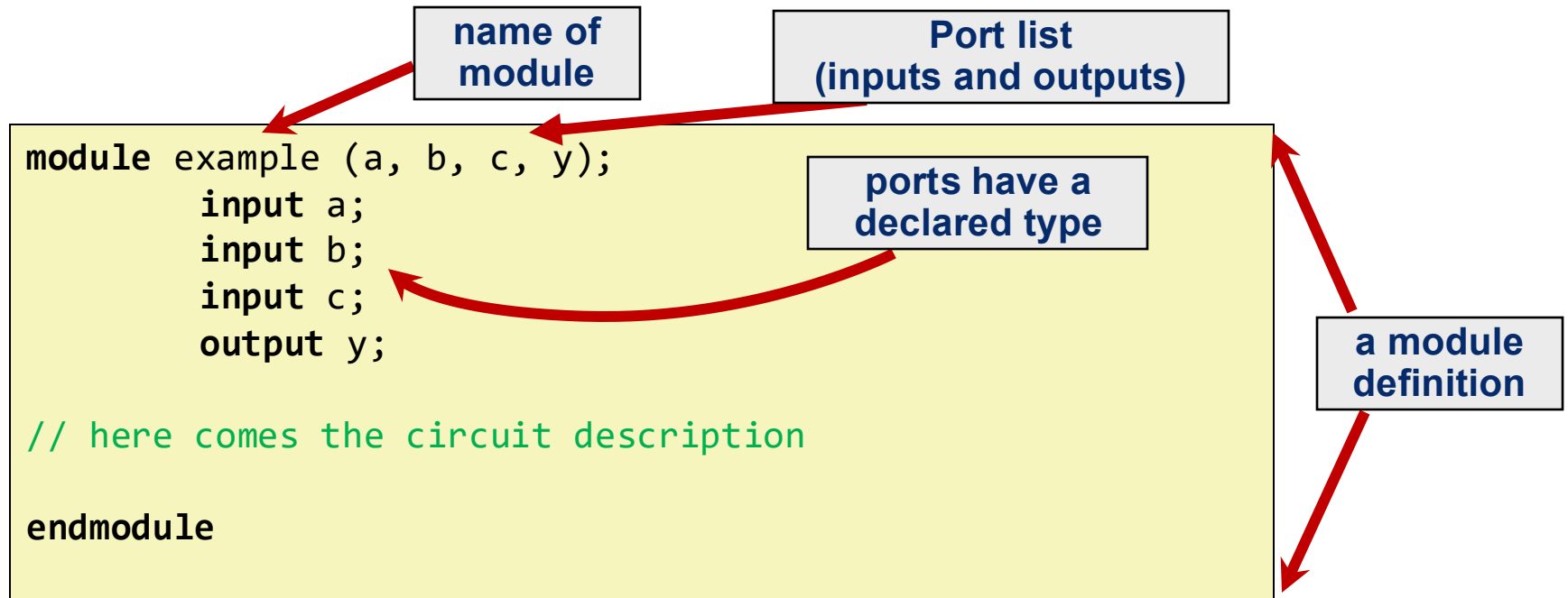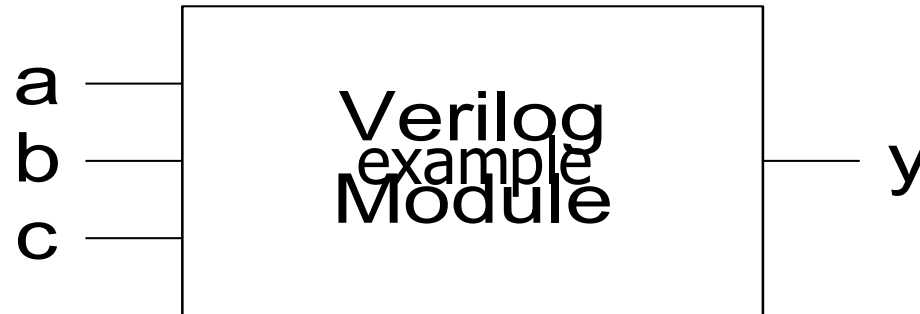

A Question of Style (and Consistency)

- **The following two codes are functionally identical**

```
module test ( a, b, y );  
    input a;  
    input b;  
    output y;  
  
endmodule
```

```
module test ( input a,  
              input b,  
              output y );  
  
endmodule
```

port name and direction declaration
can be combined

What If We Have Multi-bit Input/Output?

- **You can also define multi-bit Input/Output (Bus)**

- [range_end : range_start]
- **Number of bits:** range_end – range_start + 1


- **Example:**

```
input  [31:0] a;    // a[31], a[30] .. a[0]
output [15:8] b1;   // b1[15], b1[14] .. b1[8]
output [7:0]  b2;   // b2[7], b2[6] .. b2[0]
input           c;  // single signal
```

- **a** represents a 32-bit value, so we prefer to define it as:
[31:0] a
- It is preferred over [0:31] a which resembles *array* definition
- It is good practice to **be consistent** with the representation of multi-bit signals, i.e., always [31:0] or always [0:31]

Manipulating Bits

 - Bit Slicing
- Concatenation
- Duplication



Basic Syntax

- Verilog is case sensitive
 - `SomeName` and `somename` are not the same!
- Names cannot start with numbers:
 - `2good` is not a valid name
- Whitespaces are ignored

```
// Single line comments start with a //  
  
/* Multiline comments  
   are defined like this */
```


Two Main Styles of HDL Implementation

■ **Structural (Gate-Level)**

- ❑ The module body contains **gate-level description** of the circuit
- ❑ Describe how modules are interconnected
- ❑ Each module contains other modules (instances)
- ❑ ... and interconnections between those modules
- ❑ Describes a hierarchy of modules defined as gates


■ **Behavioral**

- ❑ The module body contains **functional description** of the circuit
- ❑ Contains logical and mathematical **operators**
- ❑ **Level of abstraction is higher than gate-level**
 - Many possible gate-level realizations of a behavioral description

■ **Many practical designs use a combination of both**

Structural (Gate-Level) HDL

Structural HDL: Instantiating a Module

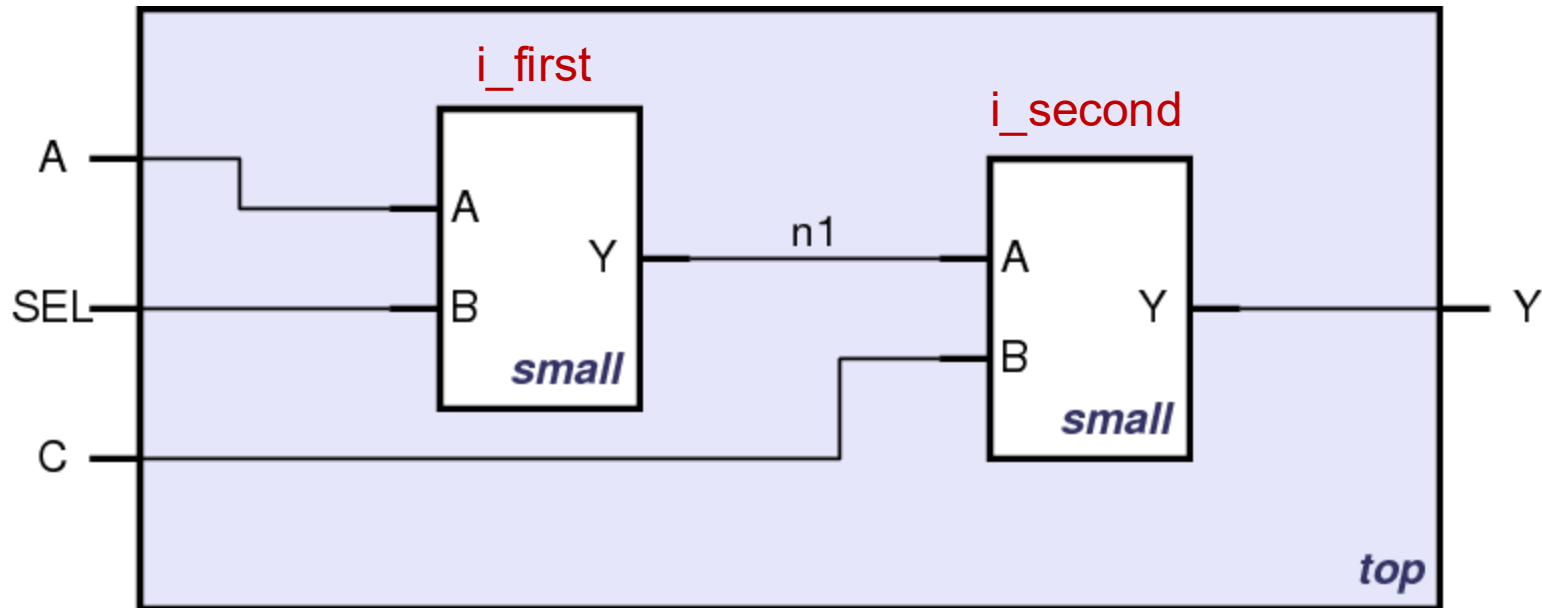


Schematic of module "top" that is built from two instances of module "small"

Structural HDL Example

■ Module Definitions in Verilog
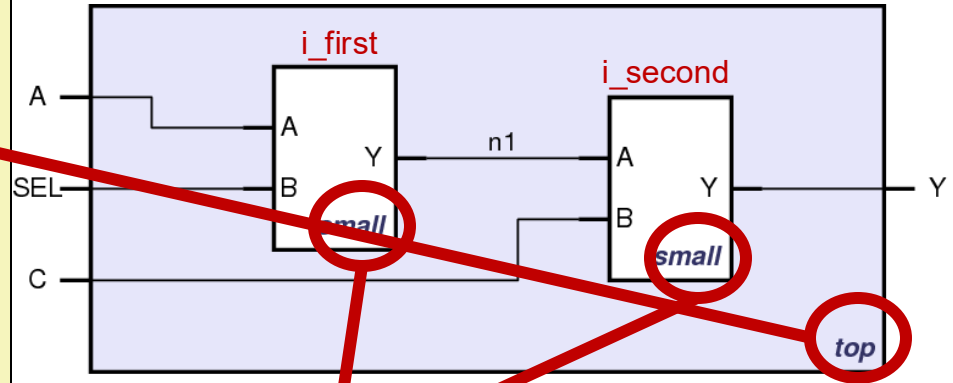
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
endmodule
```




```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Structural HDL Example

■ Defining wires (module interconnections)

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

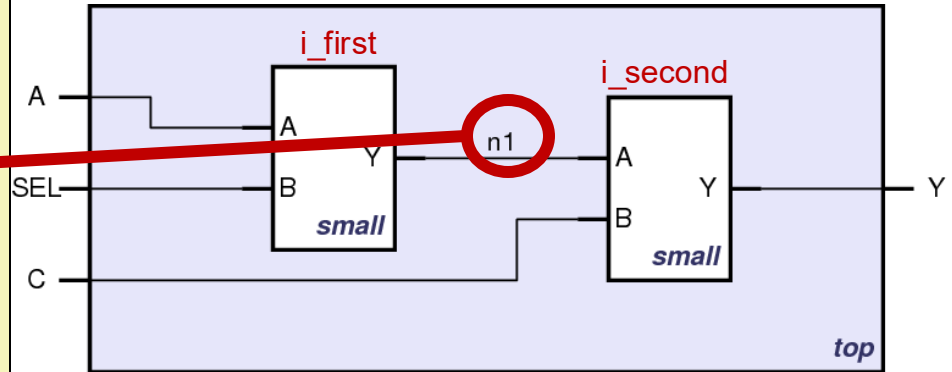

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


Structural HDL Example

■ The first instantiation of the “small” module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
// instantiate small once  
small i_first ( .A(A),  
                .B(SEL),  
                .Y(n1) );
```

```
endmodule
```

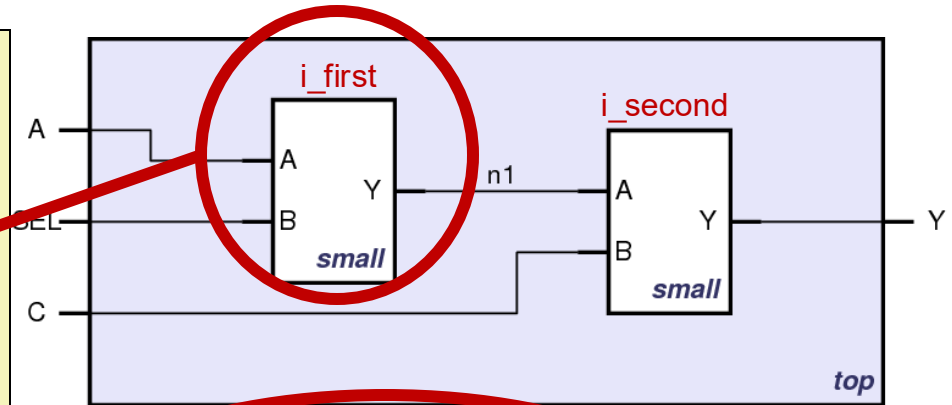

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```

Structural HDL Example


■ The second instantiation of the “small” module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );
```

```
  // instantiate small second time  
  small i_second ( .A(n1),  
                   .B(C),  
                   .Y(Y) );
```

```
endmodule
```

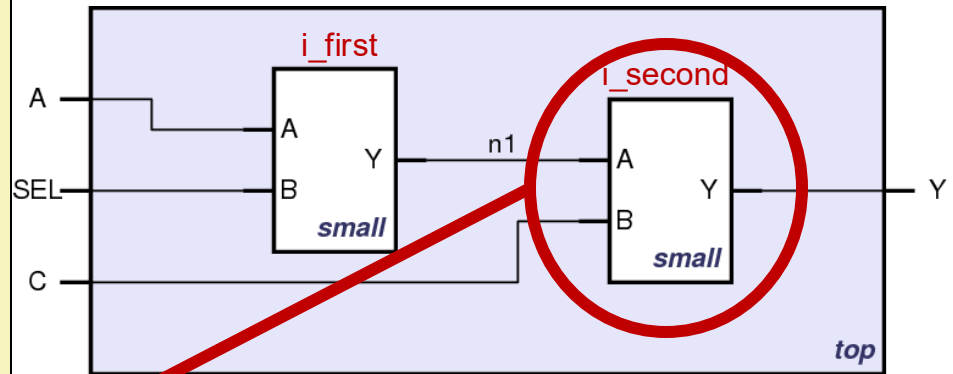

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
  // description of small
```

```
endmodule
```


Structural HDL Example

■ Short form of module instantiation


```
module top (A, SEL, C, Y);
  input A, SEL, C;
  output Y;
  wire n1;

  // alternative short form
  small i_first ( A, SEL, n1 );

  /* In the short form above,
     pin order is very important */

  // safer choice; any pin order
  small i_second ( .B(C),
                  .Y(Y),
                  .A(n1) );

endmodule
```

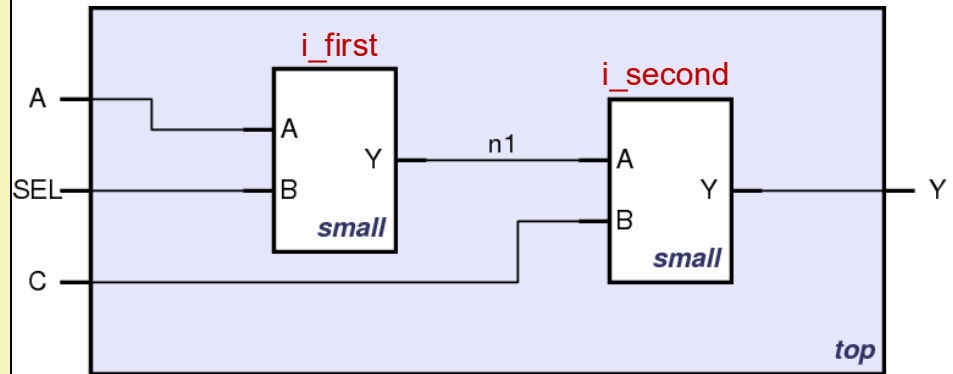

```
module small (A, B, Y);
  input A;
  input B;
  output Y;



  // description of small

endmodule
```

**Short form is not good practice
as it reduces code maintainability**

Recall: Multiplexer (MUX), or Selector (II)

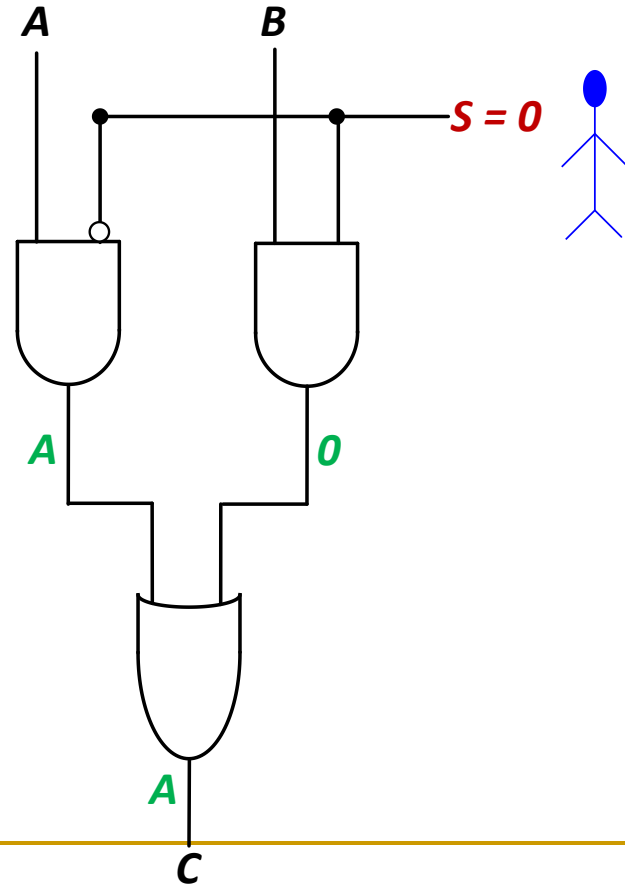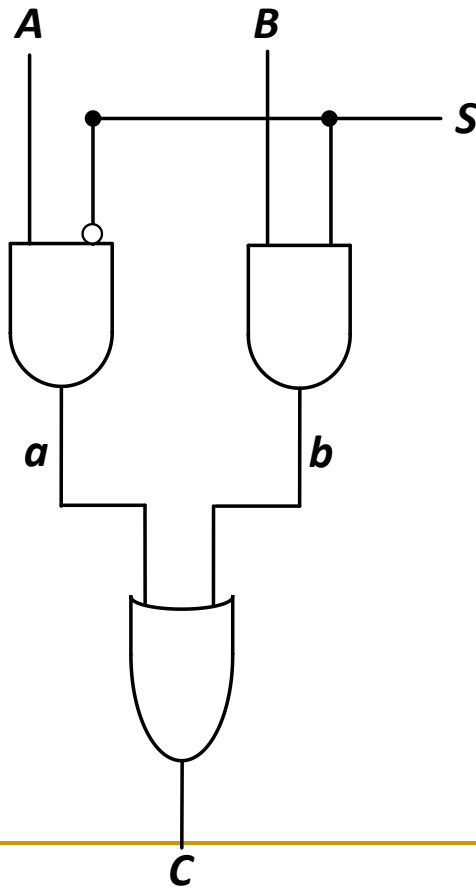
- **Selects** one of the N inputs to connect it to the output
 - based on the value of a $\log_2 N$ -bit control input called **select**
- Example: 2-to-1 MUX



Structural HDL Example (II)

- Verilog supports basic logic gates as predefined *primitives*
 - These primitives are *instantiated* like modules except that they are predefined in Verilog and *do not need a module definition*
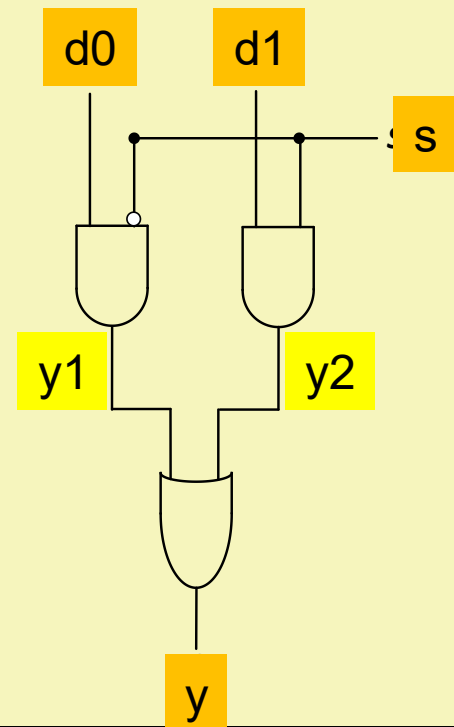
```
module mux2(input d0, d1,  
            input s,  
            output y);  
    wire ns, y1, y2;  
  
    not    g1 (ns, s);  
    and    g2 (y1, d0, ns);  
    and    g3 (y2, d1, s);  
    or     g4 (y, y1, y2);  
  
endmodule
```



Behavioral HDL

Recall: Two Main Styles of HDL Implementation

■ **Structural (Gate-Level)**

- ❑ The module body contains **gate-level description** of the circuit
- ❑ Describe how modules are interconnected
- ❑ Each module contains other modules (instances)
- ❑ ... and interconnections between those modules
- ❑ Describes a hierarchy of modules defined as gates

■ **Behavioral**

- ❑ The module body contains **functional description** of the circuit
- ❑ Contains logical and mathematical **operators**
- ❑ **Level of abstraction is higher than gate-level**
 - Many possible gate-level realizations of a behavioral description


■ **Many practical designs use a combination of both**

Behavioral HDL: Defining Functionality

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
    assign y = ~a & ~b & ~c |  
               a & ~b & ~c |  
               a & ~b & c;  
  
endmodule
```

Behavioral HDL: Schematic View

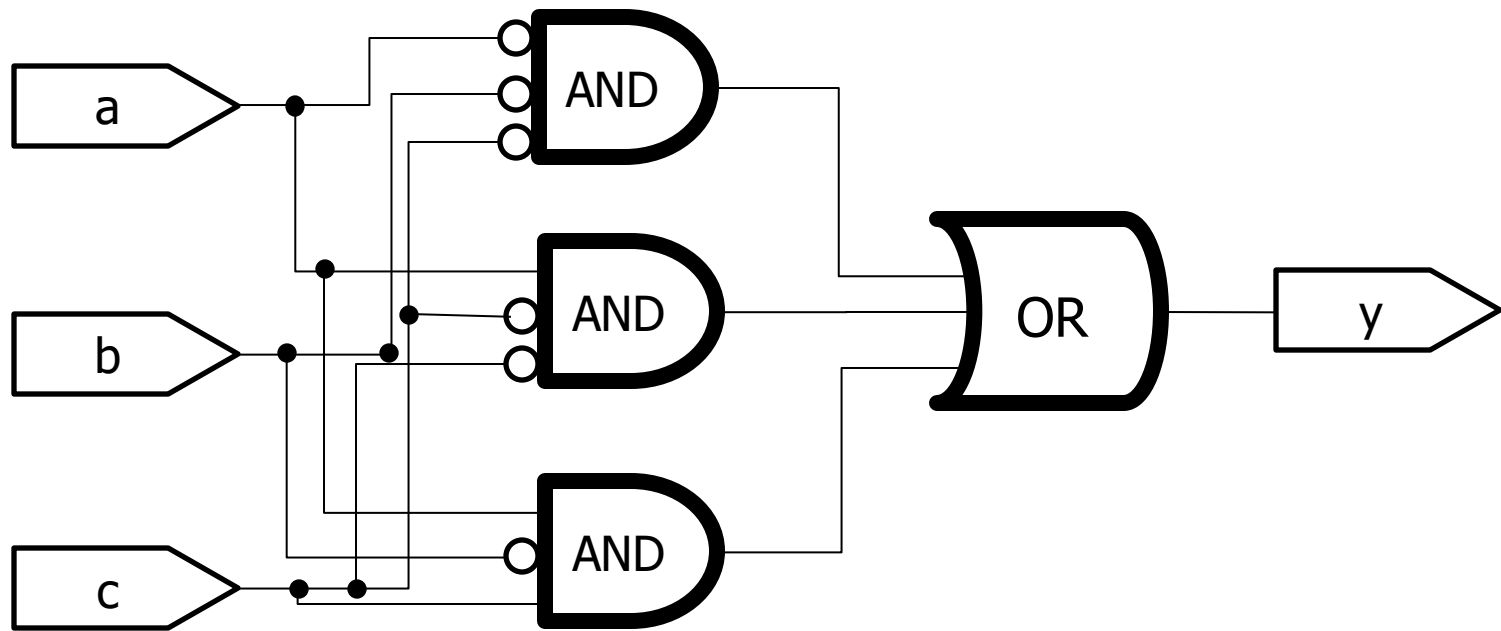A behavioral implementation still models a hardware circuit!



Bitwise Operators in Behavioral Verilog


```
module gates(input  [3:0]  a, b,  
              output [3:0] y1, y2, y3, y4, y5);
```

```
    /* Five different two-input logic  
       gates acting on 4 bit buses */
```

```
    assign y1 = a & b;      // AND  
    assign y2 = a | b;      // OR  
    assign y3 = a ^ b;      // XOR  
    assign y4 = ~(a & b);   // NAND  
    assign y5 = ~(a | b);   // NOR
```

```
endmodule
```



Bitwise Operators: Schematic View

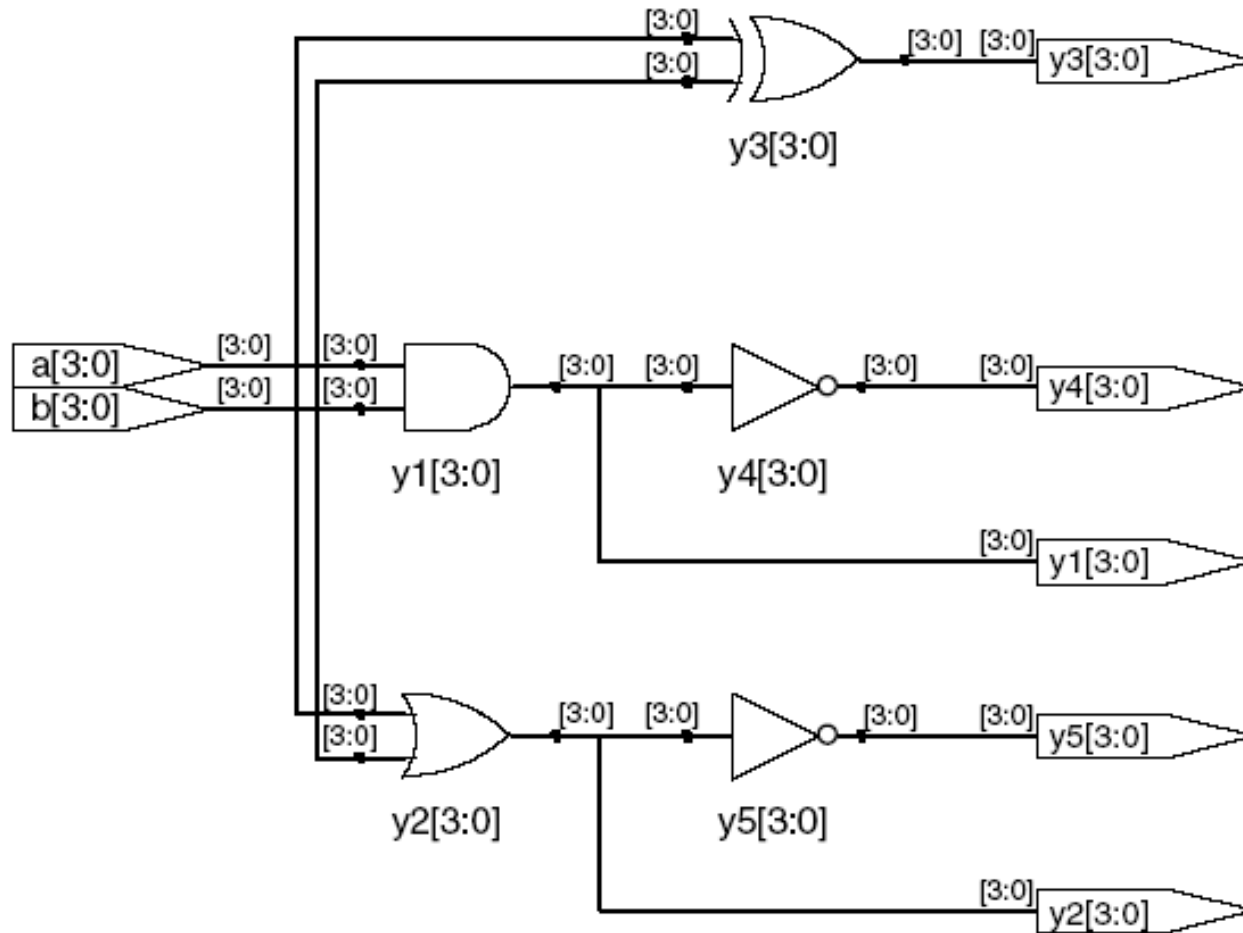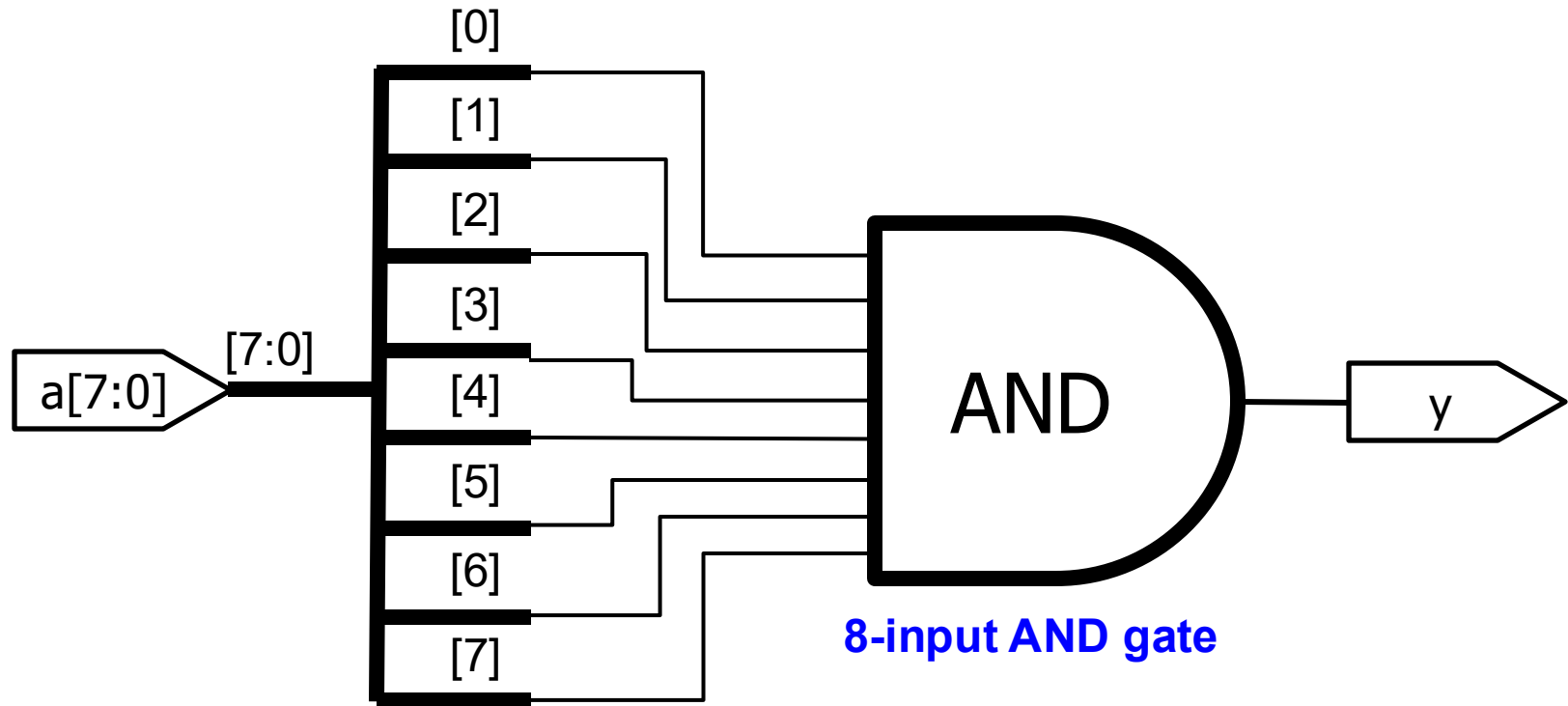

Reduction Operators in Behavioral Verilog

```
module and8(input  [7:0] a,  
            output          y);  
  
    assign y = &a;  
  
    // &a is much easier to write than  
    // assign y = a[7] & a[6] & a[5] & a[4] &  
    //             a[3] & a[2] & a[1] & a[0];  
  
endmodule
```

Reduction Operators: Schematic View




Conditional Assignment in Behavioral Verilog

```
module mux2(input  [3:0] d0, d1,  
            input      s,  
            output [3:0] y);  
  
    assign y = s ? d1 : d0;  
    // if (s) then y=d1 else y=d0;  
  
endmodule
```

- ? : is also called a **ternary operator** as it operates on three inputs:
 - ❑ s
 - ❑ d1
 - ❑ d0

Conditional Assignment: Schematic View

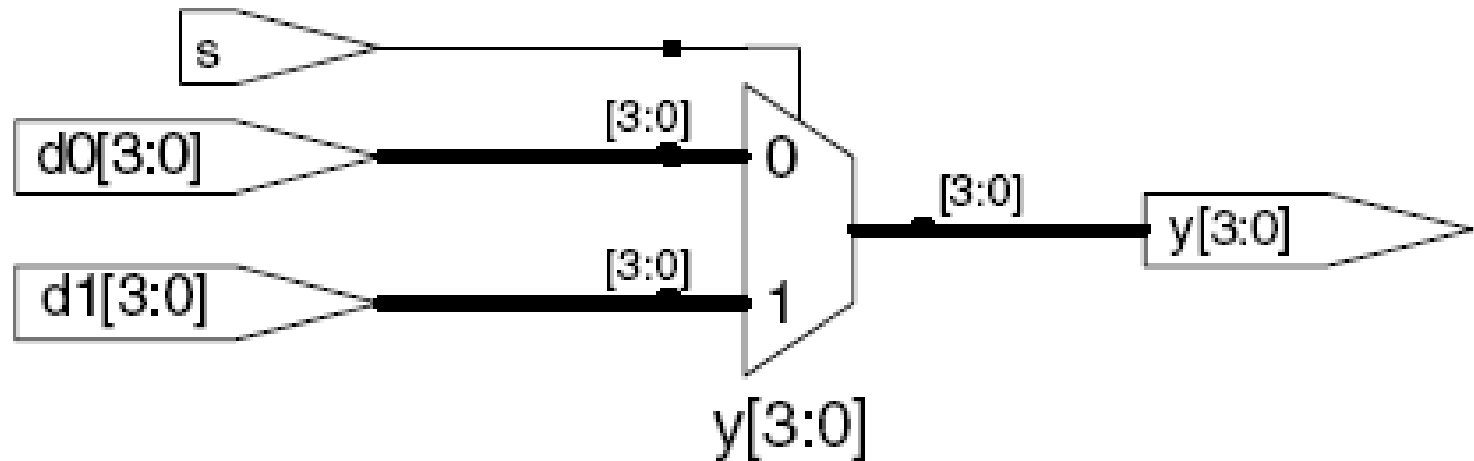

More Complex Conditional Assignments

```
module mux4(input  [3:0] d0, d1, d2, d3
            input  [1:0] s,
            output [3:0] y);

    assign y = s[1] ? ( s[0] ? d3 : d2)
                : ( s[0] ? d1 : d0);

    // if (s1) then
    //     if (s0) then y=d3 else y=d2
    // else
    //     if (s0) then y=d1 else y=d0

endmodule
```

Even More Complex Conditional Assignments



```
module mux4(input  [3:0] d0, d1, d2, d3
            input  [1:0] s,
            output [3:0] y);

    assign y = (s == 2'b11) ? d3 :
               (s == 2'b10) ? d2 :
               (s == 2'b01) ? d1 :
               d0;

    // if      (s = "11" ) then y= d3
    // else if (s = "10" ) then y= d2
    // else if (s = "01" ) then y= d1
    // else                      y= d0

endmodule
```

Recall: A 4-to-1 Multiplexer

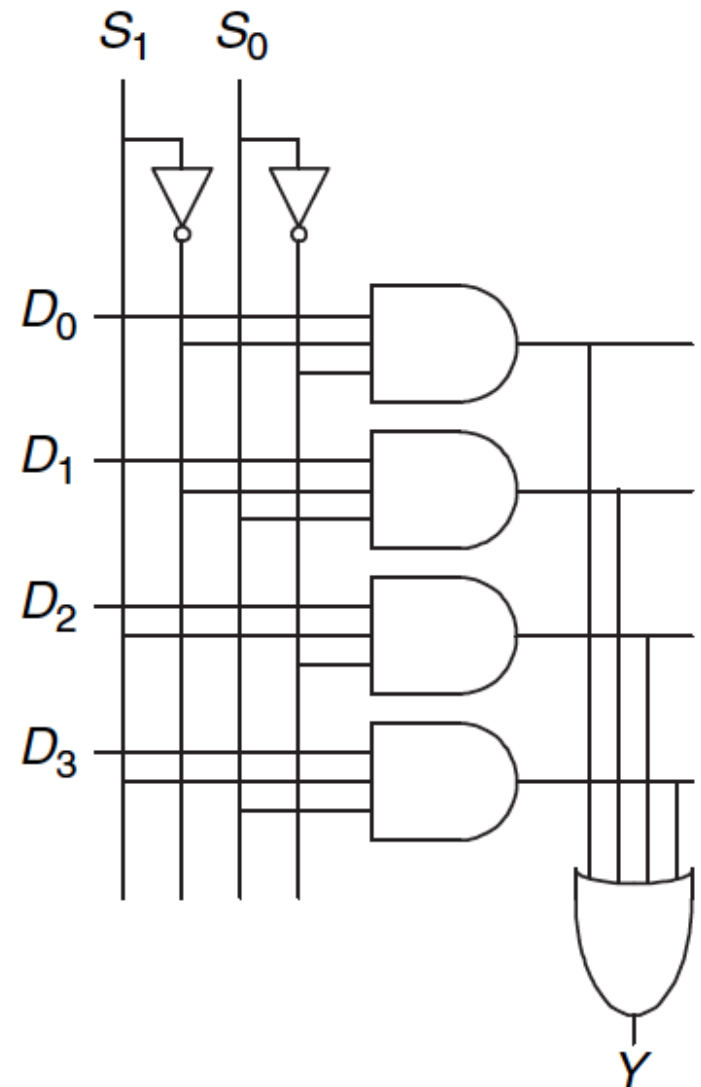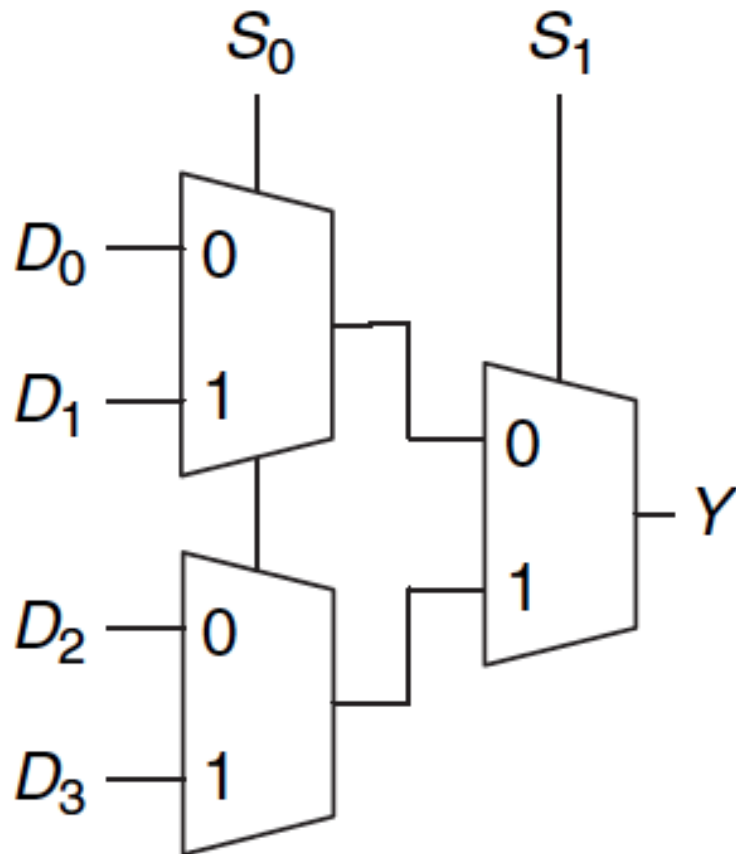

Precedence of Operations in Verilog

Highest

~	NOT
*, /, %	mult, div, mod
+, -	add, sub
<<, >>	shift
<<<, >>>	arithmetic shift
<, <=, >, >=	comparison
==, !=	equal, not equal
&, ~&	AND, NAND
^, ~^	XOR, XNOR
, ~	OR, NOR
?:	ternary operator

Lowest

How to Express Numbers?

N' Bxx

8' b0000_0001

- (N) Number of bits

- Expresses how many bits will be used to store the value

- (B) Base

- Can be b (binary), h (hexadecimal), d (decimal), o (octal)

- (xx) Number

- The value expressed in base
- Can also have X (invalid) and Z (floating), as values
- Underscore _ can be used to improve readability

Number Representation in Verilog

Verilog	Stored Number	Verilog	Stored Number
4'b1001	1001	4'd5	0101
8'b1001	0000 1001	12'hFA3	1111 1010 0011
8'b0000_1001	0000 1001	8'o12	00 001 010
8'bxX0X1zZ1	XX0X 1ZZ1	4'h7	0111
'b01	0000 .. 0001	12'h0	0000 0000 0000




**32 bits
(default)**

Reminder: Floating Signals (Z)

- **Floating signal:** Signal that is not driven by any circuit
 - Open circuit, floating wire
- Also known as: **high impedance, hi-Z, tri-stated** signals

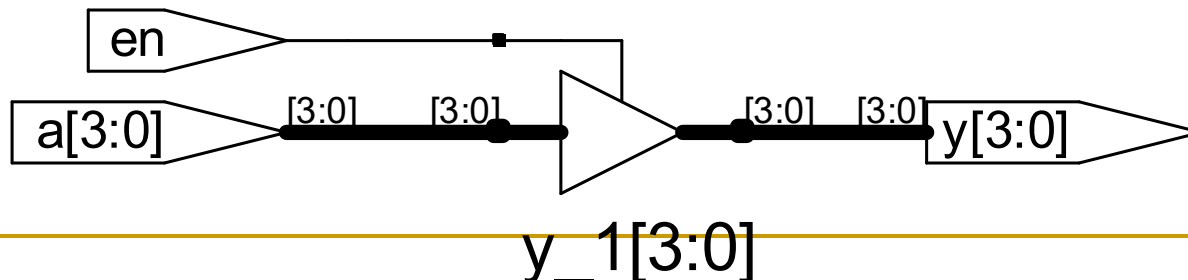
```
module tristate_buffer(input  [3:0] a,  
                      input    en,  
                      output [3:0] y);  
  
    assign y = en ? a : 4'bz;  
  
endmodule
```



Recall: Tri-State Buffer

- A tri-state buffer enables gating of different signals onto a wire

Tristate
Buffer

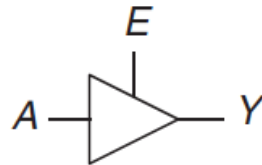

<i>E</i>	<i>A</i>	<i>Y</i>
0	0	Z
0	1	Z
1	0	0
1	1	1

**A tri-state buffer
acts like a switch**


Figure 2.40 Tristate buffer

- **Floating signal (Z):** Signal that is not driven by any circuit
 - Open circuit, floating wire


Recall: Example: Use of Tri-State Buffers

- Imagine a wire connecting the CPU and memory
 - At any time only the CPU or the memory can place a value on the wire, both not both
 - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time

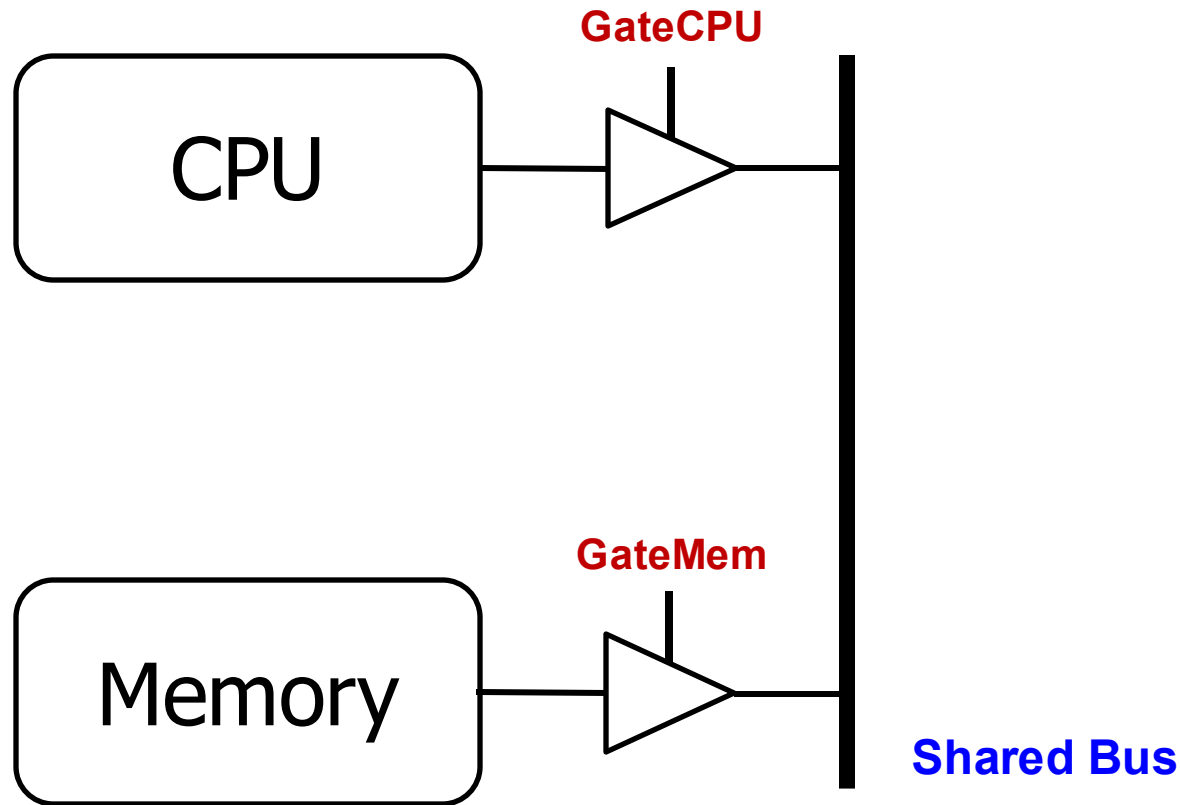Recall: Example Design with Tri-State Buffers



Recall: Another Example

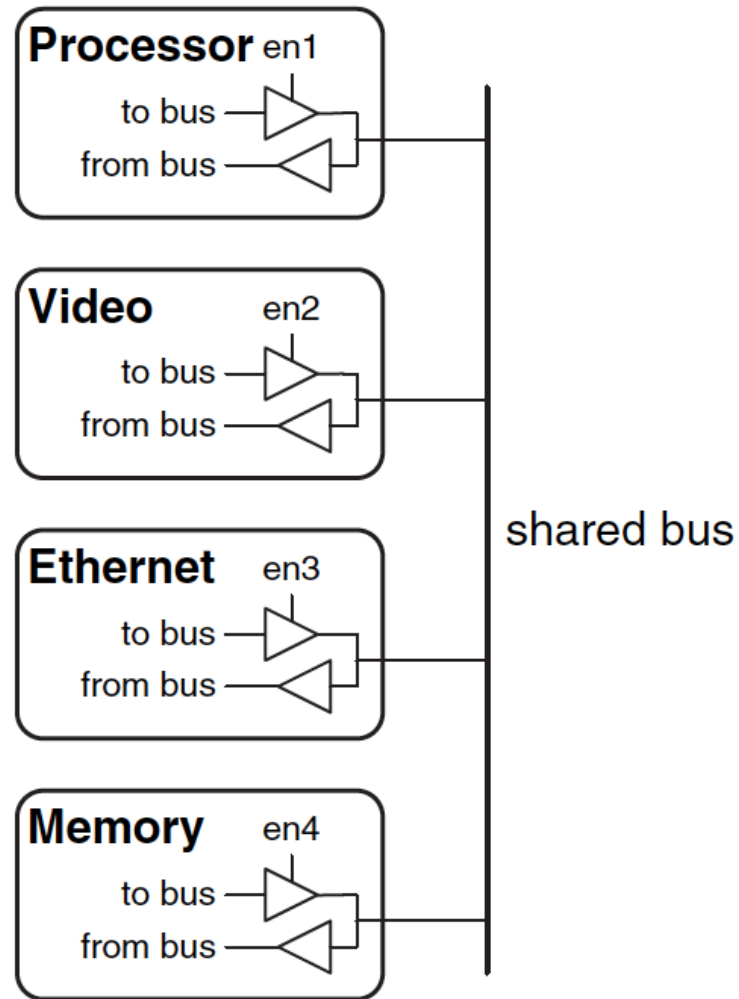

Truth Table for AND Gate with Z and X

AND		A			
		0	1	Z	X
B	0	0	0	0	0
	1	0	1	X	X
	Z	0	X	X	X
	X	0	X	X	X


Recall: Simplified Priority Circuit

- Priority Circuit
 - ❑ Inputs: “Requestors” with priority levels
 - ❑ Outputs: “Grant” signal for each requestor
 - ❑ Example 4-bit priority circuit

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

Figure 2.29 Priority circuit truth table with don't cares (X's)

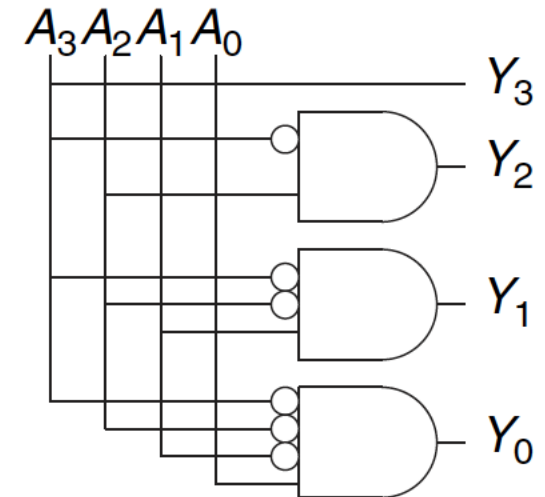

X (Don't Care) means *I don't care what the value of this input is*

What Happens with HDL Code?

■ Synthesis (i.e., Hardware Synthesis)

- ❑ Modern tools are able to **map** ***synthesizable** HDL code* into low-level *cell libraries* → *netlist describing gates and wires*
- ❑ They can perform many **optimizations**
- ❑ ... however they **can not guarantee** that a solution is optimal
 - Mainly due to **computationally expensive** **placement** and **routing** algorithms
 - Need to describe your circuit in HDL in a nice-to-synthesize way
- ❑ Most common way of Digital Design these days


■ Simulation

- ❑ Allows the behavior of the circuit to be **verified without actually manufacturing the circuit**
- ❑ Simulators can work on *structural* or *behavioral* HDL
- ❑ Simulation is essential for functional and timing verification



Recall This “example”

```
module example (a, b, c, y);  
    input a;  
    input b;  
    input c;  
    output y;  
  
    // here comes the circuit description  
    assign y = ~a & ~b & ~c |  
               a & ~b & ~c |  
               a & ~b & c;  
  
endmodule
```

Synthesizing the “example”

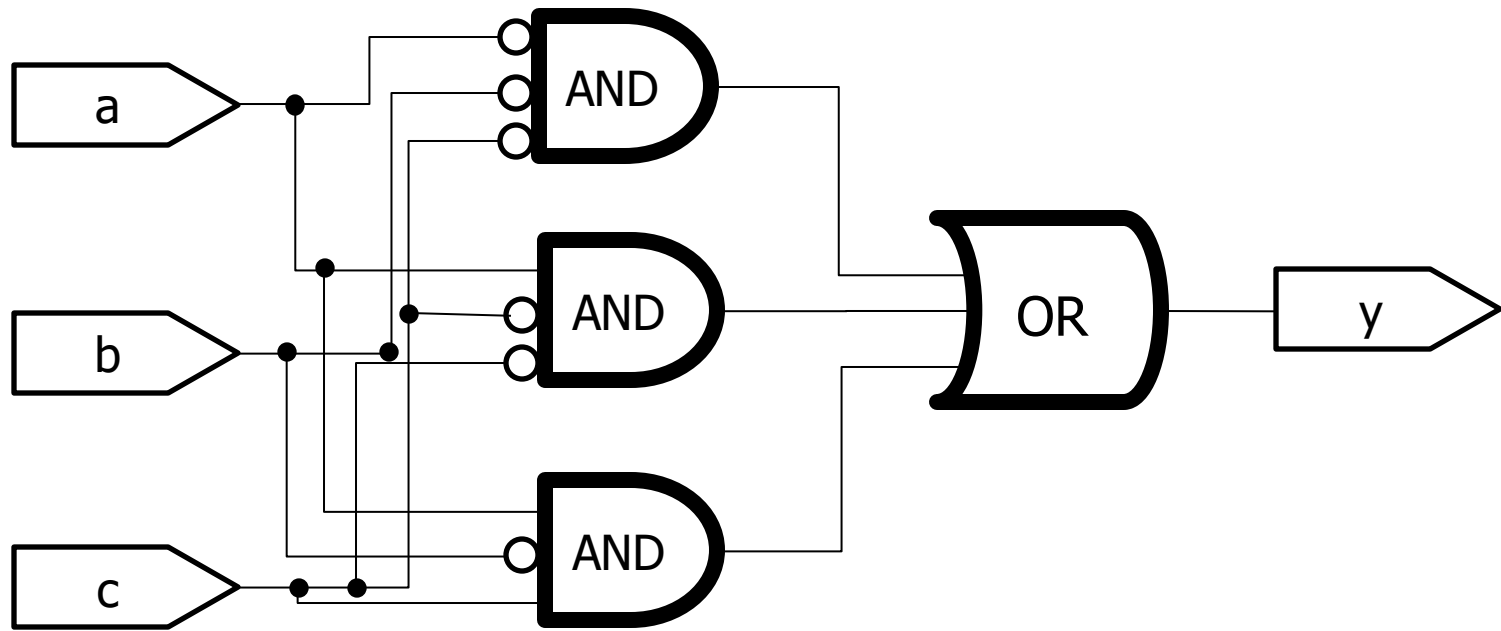

Simulating the “example”

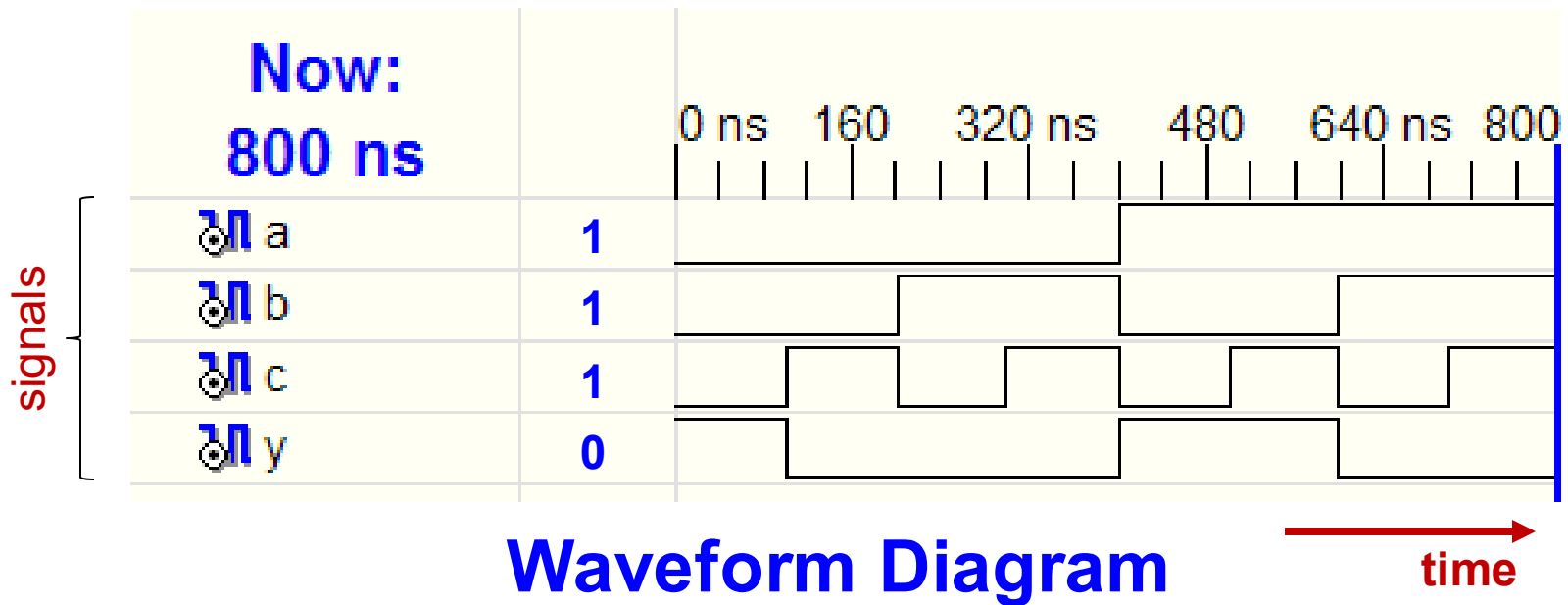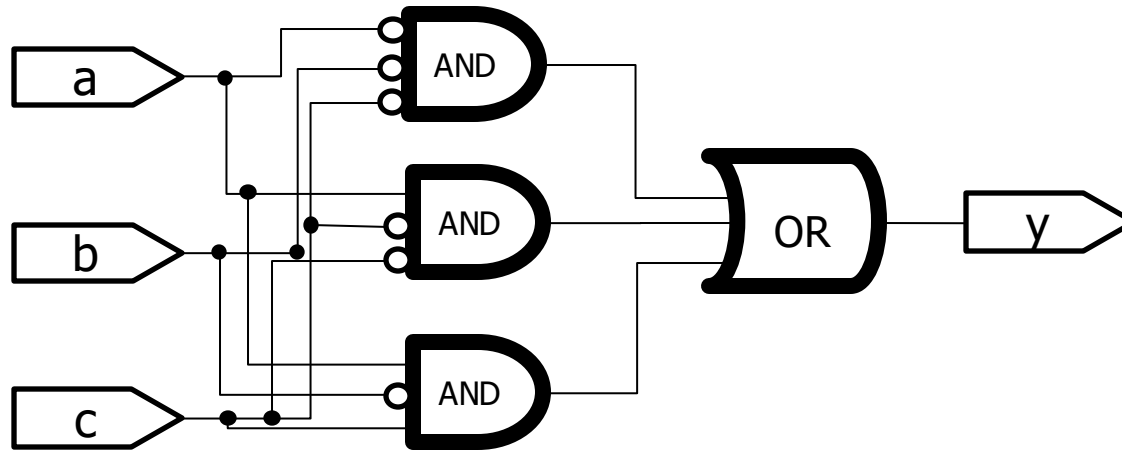

A Note on Hardware Synthesis

One of the most common mistakes for beginners is to think of HDL as a computer program rather than as a shorthand for describing digital hardware. If you don't know approximately what hardware your HDL should synthesize into, you probably won't like what you get. You might create far more hardware than is necessary, or you might write code that simulates correctly but cannot be implemented in hardware. Instead, think of your system in terms of blocks of combinational logic, registers, and finite state machines. Sketch these blocks on paper and show how they are connected before you start writing code.

What We Have Seen So Far

- **Describing structural hierarchy with Verilog**
 - Instantiate modules in an other module
- **Describing functionality using behavioral modeling**
- **Writing simple logic equations**
 - We can write AND, OR, XOR, ...
- **Multiplexer functionality**
 - If ... then ... else
- **We can describe constants**
- **But there is more...**

More Verilog Examples

- We can write Verilog code in many different ways
- Let's see how we can express the same functionality by developing Verilog code
 - At a low-level of abstraction
 - Poor readability
 - Easier automated optimization (especially for low-level tools)
 - At a high-level of abstraction
 - Better readability
 - More difficult automated optimization (large search space)

Comparing Two Numbers

- **Defining your own gates as new modules**
- We will use our gates to show different ways of implementing a 4-bit comparator (equality checker)

A 2-input XNOR gate



```
module MyXnor (input A, B,  
               output Z);  
  
    assign Z = ~(A ^ B); //not XOR  
  
endmodule
```

A 2-input AND gate

```
module MyAnd (input A, B,  
              output Z);  
  
    assign Z = A & B;    // AND  
  
endmodule
```

Recall: Equality Checker (Compare if Equal)

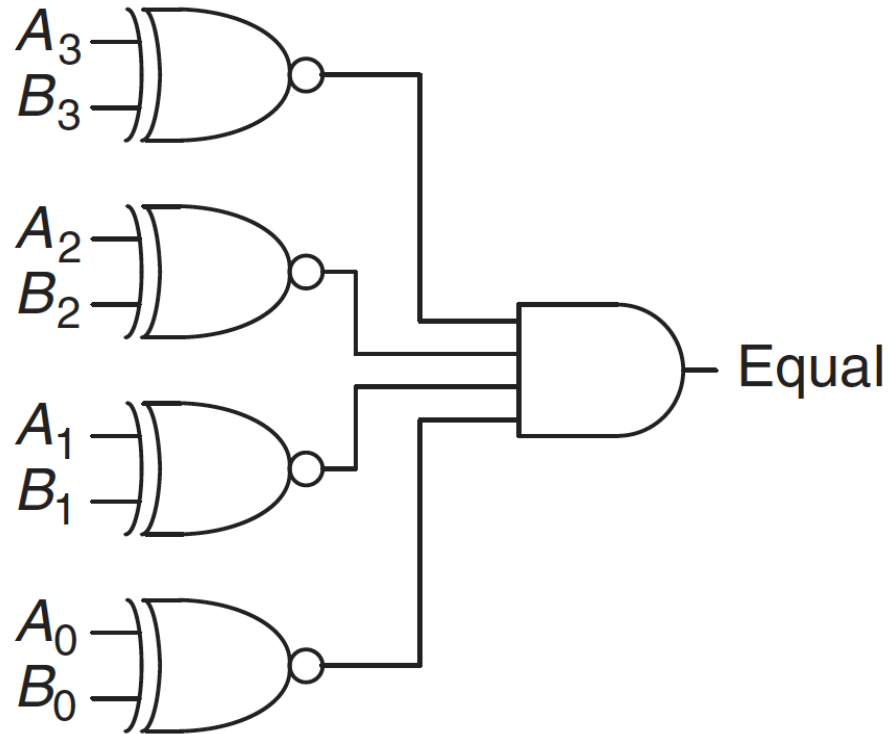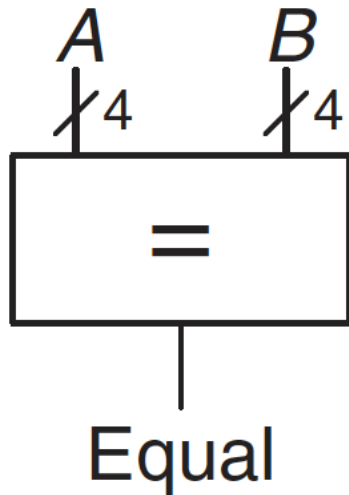- Checks if two N-input values are exactly the same
- Example: 4-bit Comparator



Gate-Level Implementation

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3, c01, c23;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    MyAnd haha (.A(c0), .B(c1), .Z(c01) ); // AND
    MyAnd hoho (.A(c2), .B(c3), .Z(c23) ); // AND
    MyAnd bubu (.A(c01), .B(c23), .Z(eq) ); // AND

endmodule
```

Using Logical Operators

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3, c01, c23;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    assign c01 = c0 & c1;
    assign c23 = c2 & c3;
    assign eq  = c01 & c23;

endmodule
```

Eliminating Intermediate Signals

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    // assign c01 = c0 & c1;
    // assign c23 = c2 & c3;
    // assign eq  = c01 & c23;
    assign eq    = c0 & c1 & c2 & c3;

endmodule
```

Multi-Bit Signals (Bus)

```
module compare (input [3:0] a, input [3:0] b,  
                output eq);  
    wire [3:0] c; // bus definition  
  
    MyXnor i0 (.A(a[0]), .B(b[0]), .Z(c[0]) ); // XNOR  
    MyXnor i1 (.A(a[1]), .B(b[1]), .Z(c[1]) ); // XNOR  
    MyXnor i2 (.A(a[2]), .B(b[2]), .Z(c[2]) ); // XNOR  
    MyXnor i3 (.A(a[3]), .B(b[3]), .Z(c[3]) ); // XNOR  
  
    assign eq  = &c; // short format  
  
endmodule
```

Bitwise Operations

```
module compare (input [3:0] a, input [3:0] b,  
                output eq);  
    wire [3:0] c; // bus definition  
  
    // MyXnor i0 (.A(a[0]), .B(b[0]), .Z(c[0]) );  
    // MyXnor i1 (.A(a[1]), .B(b[1]), .Z(c[1]) );  
    // MyXnor i2 (.A(a[2]), .B(b[2]), .Z(c[2]) );  
    // MyXnor i3 (.A(a[3]), .B(b[3]), .Z(c[3]) );  
  
    assign c = ~(a ^ b); // XNOR  
  
    assign eq = &c; // short format  
  
endmodule
```


Highest Abstraction Level: Comparing Two Numbers

```
module compare (input [3:0] a, input [3:0] b,  
               output eq);
```

```
// assign c = ~(a ^ b); // XNOR
```

```
// assign eq = &c; // short format
```

```
assign eq = (a == b) ? 1 : 0; // really short
```

```
endmodule
```

Writing More Reusable Verilog Code

- We have a module that can compare two 4-bit numbers
- What if in the overall design we need to compare:
 - **5**-bit numbers?
 - **6**-bit numbers?
 - ...
 - **N**-bit numbers?
 - Writing code for each case looks tedious
- What could be a better way?

Parameterized Modules

In Verilog, we can define **module parameters**

```
module mux2
  #(parameter width = 8)  // name and default value
  (input  [width-1:0] d0, d1,
   input                               s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```

We can set the parameters to different values
when instantiating the module

Instantiating Parameterized Modules

```
module mux2
  #(parameter width = 8) // name and default value
  (input [width-1:0] d0, d1,
   input          s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```

What About Timing?

- It is possible to define *timing relations* in Verilog. **BUT:**
 - ❑ These are **ONLY** for simulation
 - ❑ They **CAN NOT** be synthesized
 - ❑ They are used for *modeling delays* in a circuit

```
'timescale 1ns/1ps
module simple (input a, output z1, z2);

assign #5 z1 = ~a; // inverted output after 5ns
assign #9 z2 = a;  // output after 9ns

endmodule
```

More on this soon

Good Practices


- Develop/use a **consistent** naming style
- Use **MSB to LSB ordering** for buses
 - Use “**a[31:0]**”, **not** “**a[0:31]**”
- Define **one module per file**
 - Makes managing your design hierarchy easier
- Use a file name that matches module name
 - e.g., module **TryThis** is defined in a file called **TryThis.v**
- Always keep in mind that **Verilog describes hardware**

Summary (HDL for Combinational Logic)

- We have seen an overview of Verilog
- Discussed structural and behavioral modeling
- Studied combinational logic constructs

Implementing Sequential Logic Using Verilog

Sequential = Combinational + Memory

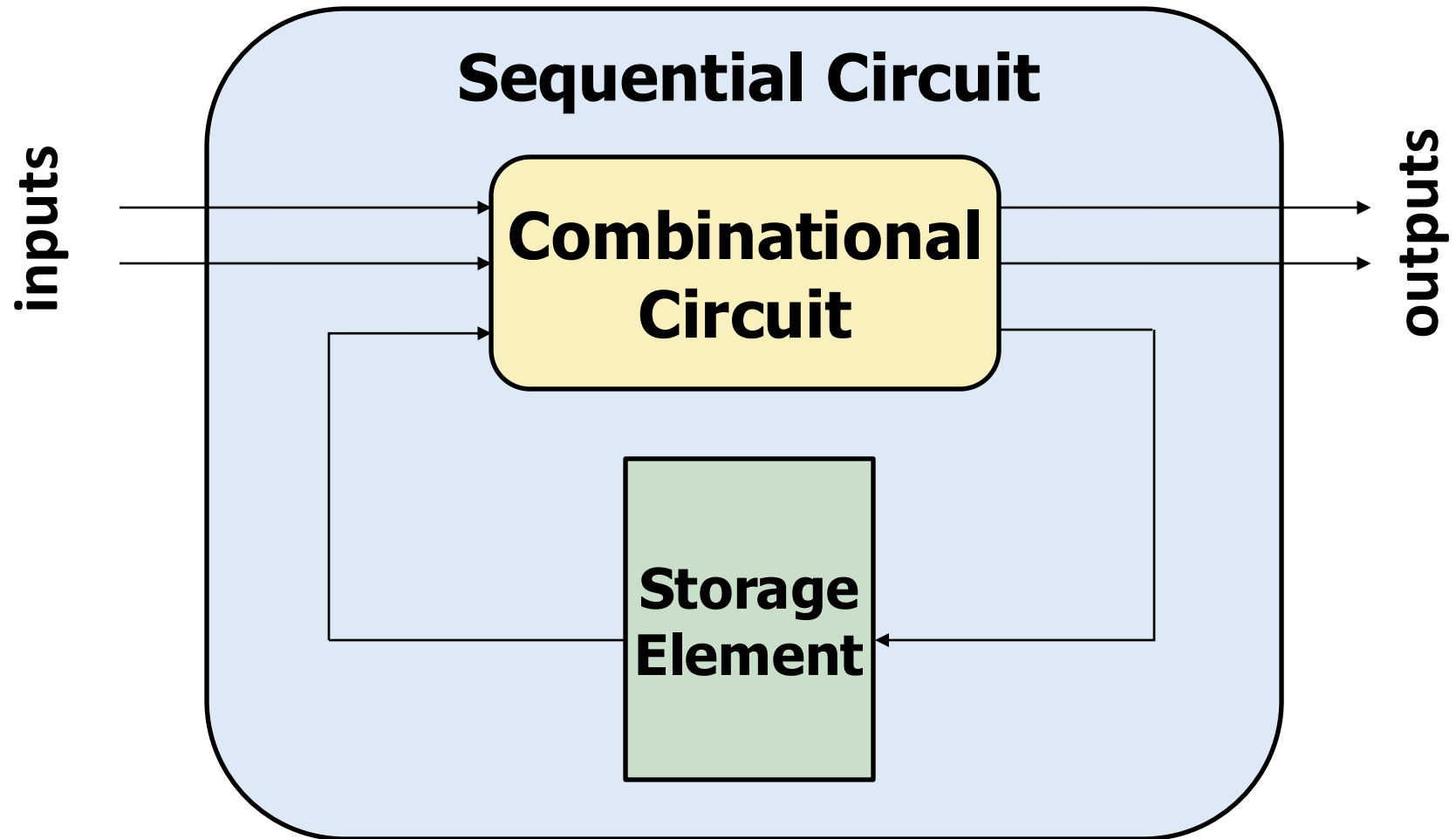

Sequential Logic in Verilog

- Define blocks that have memory
 - *Flip-Flops, Latches, Finite State Machines*
- Sequential Logic state transition is triggered by a “CLOCK” signal
 - Latches are sensitive to level of the signal
 - Flip-flops are sensitive to the transitioning (i.e., edge) of signal
- Combinational HDL constructs are **not** sufficient to express sequential logic
 - We need **new constructs**:
 - **always**
 - **posedge/negedge**


The “always” Block

```
always @ (sensitivity list)  
    statement;
```

Whenever the event in the **sensitivity list** occurs,
the statement is **executed**

Recall: The D Flip-Flop

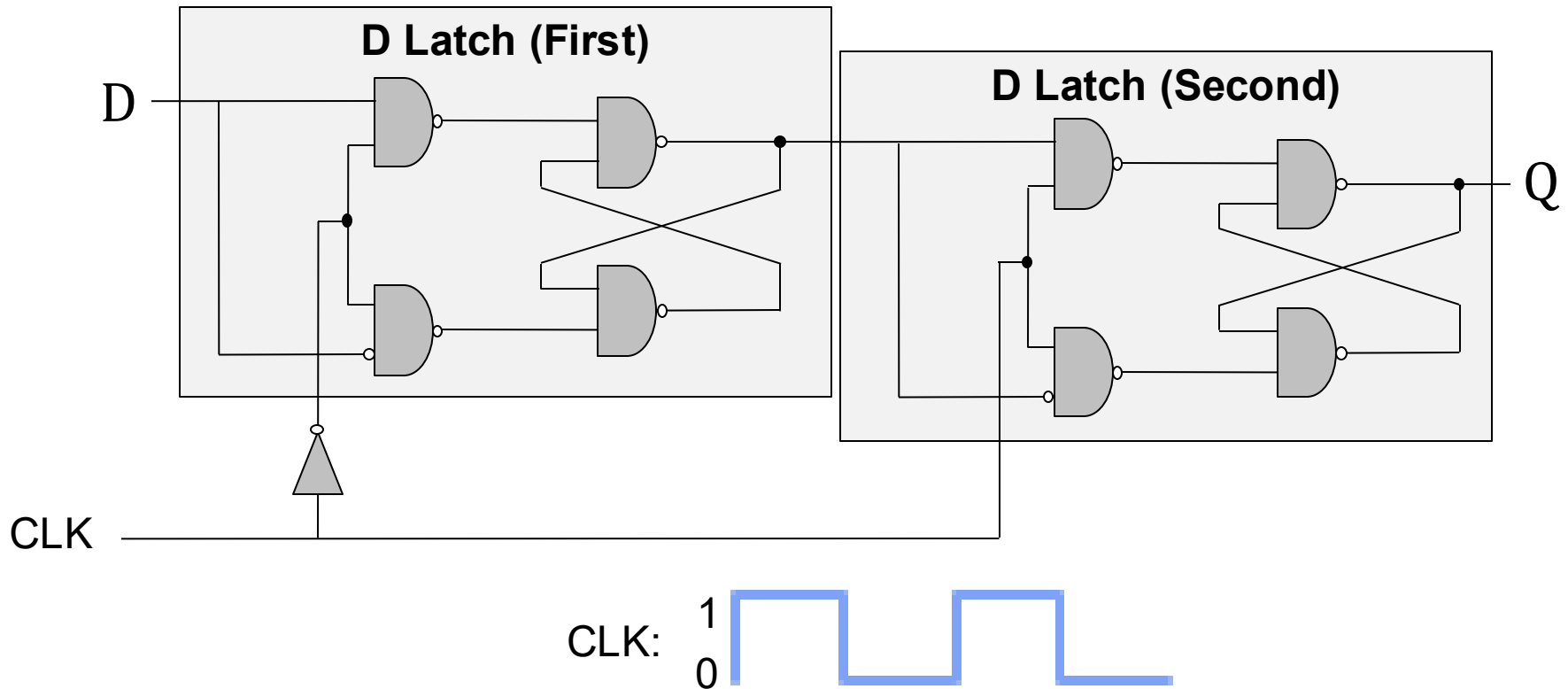
- 1) state change on clock edge, 2) data available for full cycle



- When the clock is low, 1st latch propagates **D** to the input of the 2nd (Q unchanged)
- Only when the clock is high, 2nd latch latches **D** (**Q stores D**)
 - At the rising edge of clock (clock going from 0->1), Q gets assigned D

Recall: The D Flip-Flop

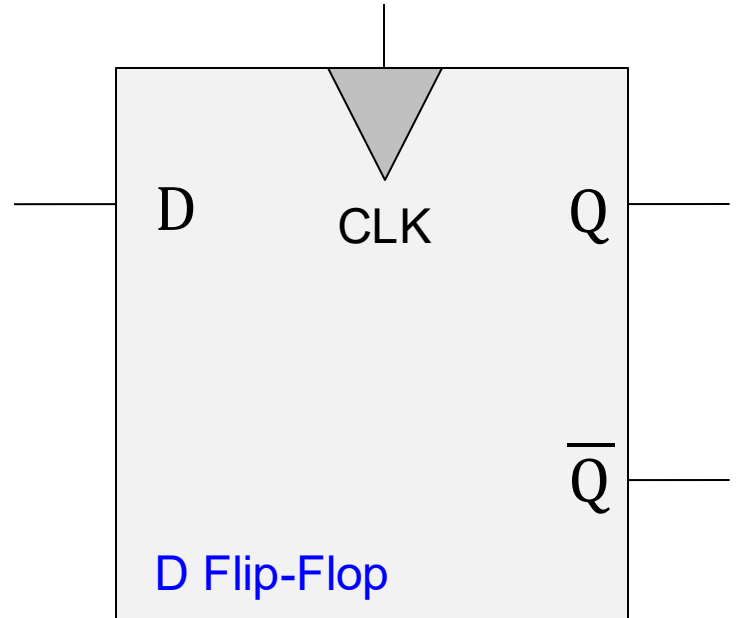
- 1) state change on clock edge, 2) data available for full cycle



- At the rising edge of clock (clock going from 0- $\rightarrow$ 1), **Q** gets assigned **D**
- At all other times, Q is unchanged

Recall: The D Flip-Flop

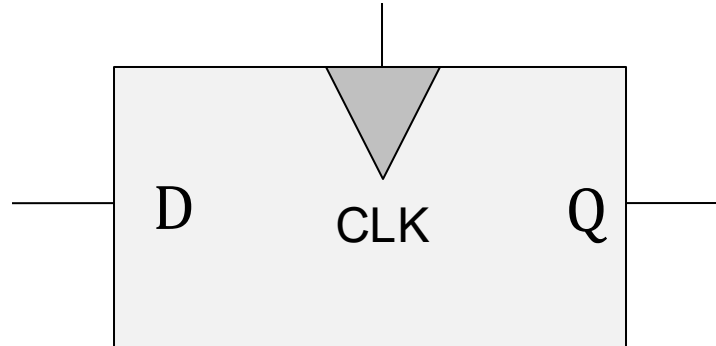- 1) state change on clock edge, 2) data available for full cycle



We can use **D Flip-Flops**
to implement the state register

- At the rising edge of clock (clock going from 0->1), **Q** gets assigned **D**
- At all other times, **Q** is unchanged

Example: D Flip-Flop

```
module flop(input          clk,  
            input    [3:0] d,  
            output reg [3:0] q);  
  
    always @ (posedge clk)  
        q <- d;           // pronounced “q gets d”  
  
endmodule
```

- **posedge** defines a rising edge (transition from 0 to 1)
- Statement executed when the **clk signal rises (posedge of clk)**
- Once the clk signal rises: the value of **d** is copied to **q**

Example: D Flip-Flop

```
module flop(input          clk,
            input          [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;                // pronounced “q gets d”

endmodule
```

- **assign** statement is **not** used within an always block
- **<=** describes a **non-blocking** assignment
 - We will see the difference between **blocking assignment** and **non-blocking** assignment soon

Example: D Flip-Flop

```
module flop(input          clk,
            input          [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;                // pronounced “q gets d”

endmodule
```

- Assigned variables need to be declared as **reg**
- The name **reg** does not necessarily mean that the value is a register (It could be, but it does not have to be)
- We will see examples later

Asynchronous and Synchronous Reset

- **Reset** signals are used to **initialize** the hardware to a known state
 - Usually activated **at system start** (on power up)
- **Asynchronous Reset**
 - The reset signal is sampled **independent of the clock**
 - Reset gets the highest priority
 - Sensitive to **glitches**, may have **metastability** issues
 - Will be discussed in the Timing & Verification Lecture
- **Synchronous Reset**
 - The reset signal is sampled **with respect to the clock**
 - The reset signal **should be active long enough** to get sampled at the clock edge
 - Results in a **completely synchronous sequential circuit**

Recall: Asynchronous vs. Synchronous State Changes

- Sequential lock we saw is an **asynchronous** “machine”
 - ❑ **State transitions occur when they occur**
 - ❑ There is nothing that synchronizes when each state transition must occur
- Most modern computers are **synchronous** “machines”
 - ❑ **State transitions take place after fixed units of time**
 - ❑ Controlled in part by a clock, as we will see soon
- **These are two different design paradigms, with tradeoffs**
 - ❑ Synchronous control can be easier to get correct when the system consists of many components and many states
 - ❑ Asynchronous control can be more efficient (no clock overheads)

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0;    // when reset
        else            q <= d;    // when clk
    end
endmodule
```

- In this example: two events can trigger the process:
 - A **rising edge** on clk
 - A **falling edge** on reset

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0;    // when reset
        else            q <= d;    // when clk
    end
endmodule
```

- For longer statements, a **begin-end** pair can be used
 - ❑ To improve readability
 - ❑ In this example, it was not necessary, but it is a good idea

D Flip-Flop with Asynchronous Reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0) q <= 0; // when reset
        else             q <= d; // when clk
    end
endmodule
```

- First **reset** is checked: if **reset** is 0, **q** is set to 0.
 - This is an **asynchronous** reset as the reset can happen **independently** of the clock (on the negative edge of reset signal)
- If there is no reset, then regular assignment takes effect

D Flip-Flop with Synchronous Reset

```
module flop_sr (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk)
    begin
        if (reset == '0') q <= 0;    // when reset
        else               q <= d;    // when clk
    end
endmodule
```

- The process is sensitive to only clock
 - Reset *happens only* when the *clock rises*. This is a *synchronous* reset

D Flip-Flop with Enable and Reset

```
module flop_en_ar (input          clk,
                  input          reset,
                  input          en,
                  input [3:0] d,
                  output reg [3:0] q);

  always @ (posedge clk, negedge reset)
  begin
    if (reset == '0') q <= 0;    // when reset
    else if (en)      q <= d;    // when en AND clk
  end
endmodule
```

- A flip-flop with **enable** and **reset**
 - Note that the **en** signal is **not** in the *sensitivity list*
- **q** gets **d** only when **clk** is rising **and** **en** is 1

Example: D Latch

```
module latch (input          clk,  
              input          [3:0] d,  
              output reg [3:0] q);  
  
    always @ (clk, d)  
        if (clk) q <= d;           // latch is transparent when  
                                    // clock is 1  
  
endmodule
```

Summary: Sequential Statements So Far

- Sequential statements are within an **always** block
- The sequential block is triggered with a change in the **sensitivity list**
- Signals assigned within an **always** must be declared as **reg**
- We use **<=** for (non-blocking) assignments and do not use **assign** within the always block.

Basics of **always** Blocks

```
module example (input          clk,
                input    [3:0] d,
                output reg [3:0] q);

    wire [3:0] normal;           // standard wire
    reg  [3:0] special;          // assigned in always

    always @ (posedge clk)
        special <= d;            // first FF array

    assign normal = ~special;    // simple assignment

    always @ (posedge clk)
        q <= normal;            // second FF array
endmodule
```

You can have as many **always** blocks as needed

Assignment to the same signal in different always blocks is not allowed!

Why Does an **always** Block Remember?

```
module flop (input          clk,
              input    [3:0] d,
              output reg [3:0] q);

    always @ (posedge clk)
        begin
            q <= d;    // when clk rises copy d to q
        end
endmodule
```

- This statement describes what happens to signal **q**
- ... but what happens when the clock is not rising?
- The value of **q** is preserved (remembered)

An **always** Block Does **NOT** Always Remember

```
module comb (input          inv,
              input    [3:0] data,
              output reg [3:0] result);

    always @ (inv, data)          // trigger with inv, data
        if (inv) result <= ~data; // result is inverted data
        else    result <= data;   // result is data

endmodule
```

- This statement describes what happens to signal **result**
 - When **inv** is 1, **result** is **~data**
 - When **inv** is not 1, **result** is **data**
- The circuit is combinational (no memory)
 - **result** is assigned a value **whenever an input value changes & in all cases of the if .. else block**

always Blocks for Combinational Circuits

- An **always** block defines **combinational logic** if:
 - All outputs are always (**continuously**) updated
 1. All right-hand side signals are in the sensitivity list
 - You can use **always @*** for short
 2. All left-hand side signals get assigned in every possible condition of **if .. else** and **case** blocks
- It is easy to make mistakes and **unintentionally describe memorizing elements** (latches)
 - **Vivado** will most likely warn you. Make sure you check the warning messages
- **Always** blocks allow powerful combinational logic statements
 - **if .. else**
 - **case**

Sequential or Combinational?

```
wire enable, data;
reg out_a, out_b;

always @ (*) begin
    out_a = 1'b0;
    if(enable) begin
        out_a = data;
        out_b = data;
    end
end
```

No assignment for ~enable

Sequential

```
wire enable, data;
reg out_a, out_b;

always @ (data) begin
    out_a = 1'b0;
    out_b = 1'b0;
    if(enable) begin
        out_a = data;
        out_b = data;
    end
end
```

Not in the sensitivity list

Sequential

The **always** Block is **NOT** Always Practical/Nice

```
reg [31:0] result;  
wire [31:0] a, b, comb;  
wire      sel,  
  
always @ (a, b, sel)    // trigger with a, b, sel  
    if (sel) result <= a; // result is a  
    else      result <= b; // result is b  
  
assign comb = sel ? a : b;
```

- Both statements describe the **same** multiplexer
- In this case, the **always** block is more work

always Block for Case Statements (Handy!)

```
module sevenssegment (input      [3:0] data,
                      output reg [6:0] segments);

  always @ ( * )                // * is short for all signals
  case (data)                   // case statement
    4'd0: segments = 7'b111_1110; // when data is 0
    4'd1: segments = 7'b011_0000; // when data is 1
    4'd2: segments = 7'b110_1101;
    4'd3: segments = 7'b111_1001;
    4'd4: segments = 7'b011_0011;
    4'd5: segments = 7'b101_1011;
    // etc etc
    default: segments = 7'b000_0000; // required
  endcase

endmodule
```

Summary: **always** Block

- `if .. else` can **only** be used in `always` blocks
- The `always` block is **combinational** only if all `regs` within the block are always assigned to a signal
 - Use the `default` case to make sure you do not forget an unimplemented case, which may otherwise result in a latch
- Use `casex` statement to be able to check for don't cares

Non-Blocking and Blocking Assignments

Non-blocking (<=)

```
always @ (a)
begin
    a <= 2'b01;
    b <= a;
// all assignments are made here
// b is not (yet) 2'b01
end
```

- All assignments are made at the end of the block
- All assignments are made in parallel, process flow is **not-blocked**

Blocking (=)

```
always @ (a)
begin
    a = 2'b01;
// a is 2'b01
    b = a;
// b is now 2'b01 as well
end
```

- Each assignment is made immediately
- Process waits until the first assignment is complete, it **blocks** progress
- Similar to sequential programs

Why Use (Non)-Blocking Statements

- Non-blocking statements allow operating on “old” values
 - Enable easy **sequential logic** descriptions
 - Blocking statements allow a sequence of operations
 - Allow operating on immediately updated values
 - More like a “software” programming language
 - If the sensitivity list is correct, a block with non-blocking statements will **eventually** evaluate to the same result as the same block with blocking statements
 - This may require some additional iterations
-

Example: Blocking Assignment

- Assume all inputs are initially '0'

```
always @ ( * )  
begin  
    p    = a ^ b ;           // p    = 0    1  
    g    = a & b ;           // g    = 0    0  
    s    = p ^ cin ;        // s    = 0    1  
    cout = g | (p & cin) ;   // cout = 0    0  
end
```

- If **a** changes to '1'
 - All values are updated in order

The Same Example: Non-Blocking Assignment

- Assume all inputs are initially '0'

```
always @ ( * )  
begin  
    p    <= a ^ b ;           // p    = 0  1  
    g    <= a & b ;           // g    = 0  0  
    s    <= p ^ cin ;        // s    = 0  0  
    cout <= g | (p & cin) ;  // cout = 0  0  
end
```

- If **a** changes to '1'
 - All assignments are concurrent
 - When **s** is being assigned, **p** is still 0

The Same Example: Non-Blocking Assignment

- After the first iteration, **p** has changed to '1' as well

```
always @ ( * )
begin
    p    <= a ^ b ;           // p    = 1    1
    g    <= a & b ;           // g    = 0    0
    s    <= p ^ cin ;         // s    = 0    1
    cout <= g | (p & cin) ;    // cout = 0    0
end
```

- Since there is a change in **p**, the process **triggers again**
- This time **s** is calculated with **p=1**

Rules for Signal Assignment

- Use `always @(posedge clk)` and `non-blocking` assignments (`<=`) to model `synchronous sequential logic`


```
always @ (posedge clk)
    q <= d; // non-blocking
```

- Use continuous assignments (`assign`) to model simple combinational logic


```
assign y = a & b;
```


Rules for Signal Assignment (Cont.)

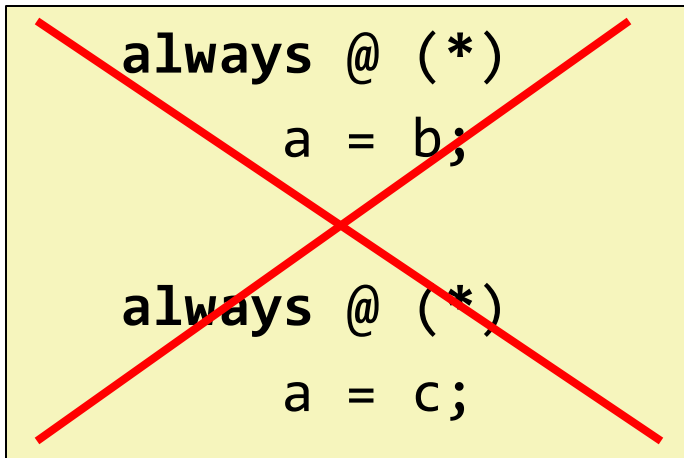- Use **always @ (*)** and **blocking** assignments (=) to model more **complicated combinational logic**
- You **cannot** make assignments to the **same** signal in more than one always block or in a *continuous assignment*



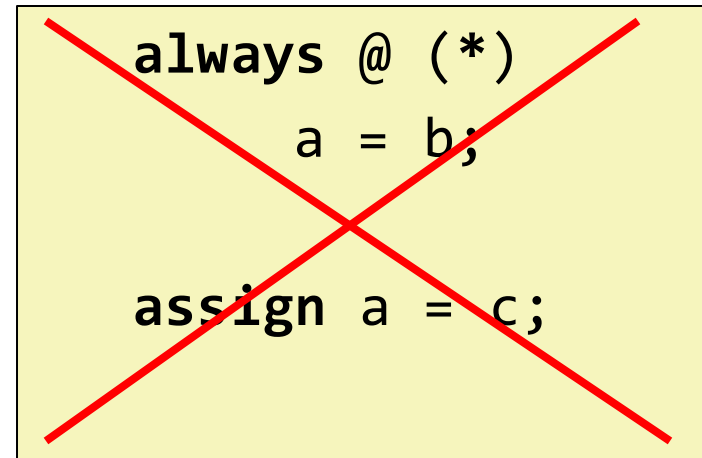
```
always @ (*)  
    a = b;  
  
always @ (*)  
    a = c;
```



```
always @ (*)  
    a = b;  
  
assign a = c;
```

Recall: Finite State Machines (FSMs)

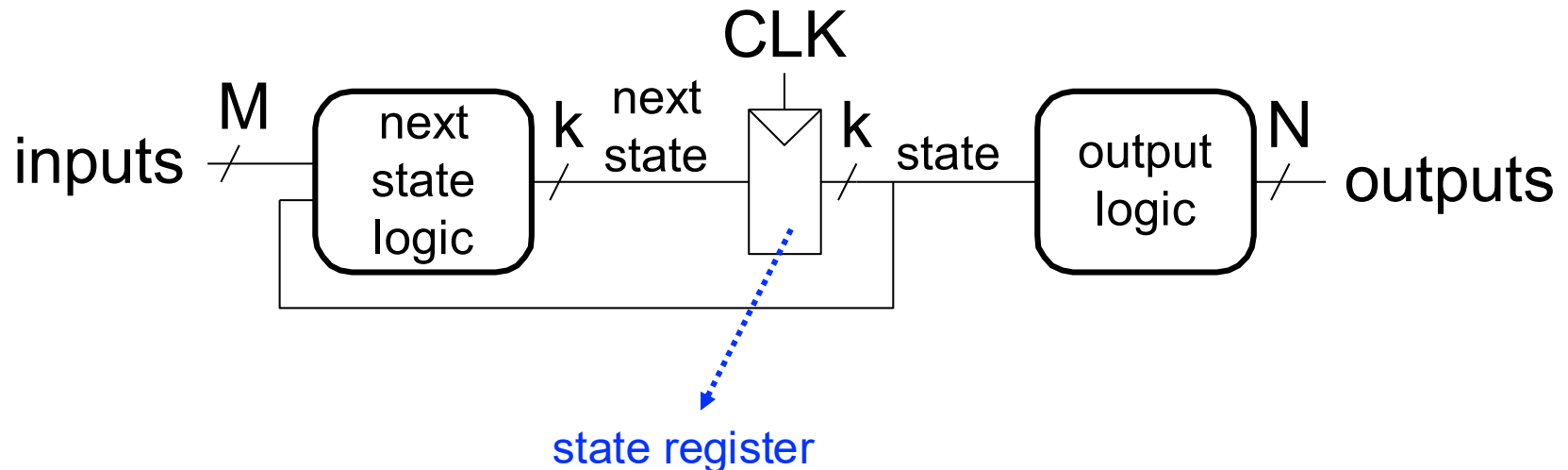- Each FSM consists of three separate parts:
 - next state logic
 - state register
 - output logic




At the beginning of the clock cycle, next state is latched into the state register

Recall: Finite State Machines (FSMs) Consist of:



■ Sequential Circuits

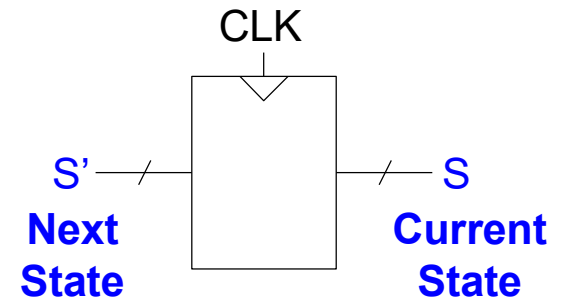- State register(s)
 - Store the current state and
 - Provide the next state at the clock edge



■ Combinational Circuits

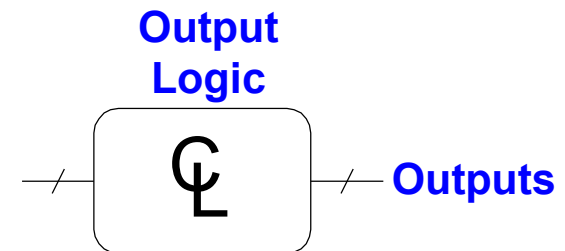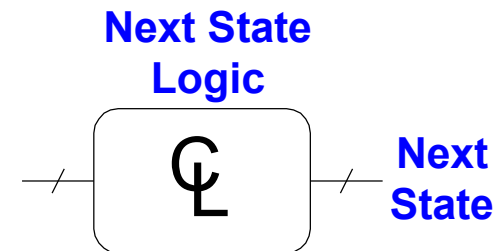
- Next state logic
 - Determines what the next state will be
- Output logic
 - Generates the outputs




Recall: FSM Design Procedure

- **Determine** all possible states of your machine
- **Develop** a **state transition diagram**
 - Generally this is done from a textual description
 - You need to 1) determine the **inputs** and **outputs** for each **state** and 2) figure out how to get from one state to another
- **Approach**
 - Start by defining the **reset state** and what happens from it – this is typically an easy point to start from
 - Then continue to add **transitions** and **states**
 - Picking **good state names** is very important
 - Building an FSM is **like** programming (but it *is not* programming!)
 - An FSM has a sequential “control-flow” like a program with conditionals and goto’s
 - The if-then-else construct is controlled by one or more inputs
 - The outputs are controlled by the state or the inputs
 - In hardware, we typically have many concurrent FSMs

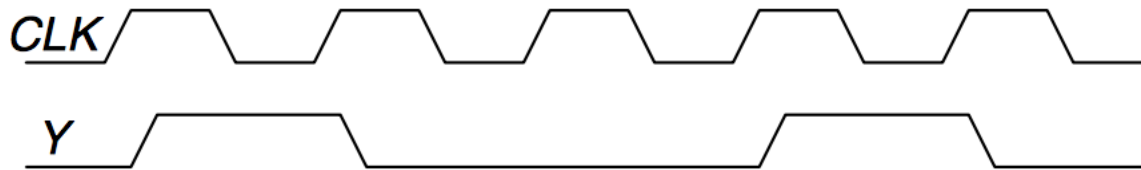FSM Example 1: Divide the Clock Frequency by 3



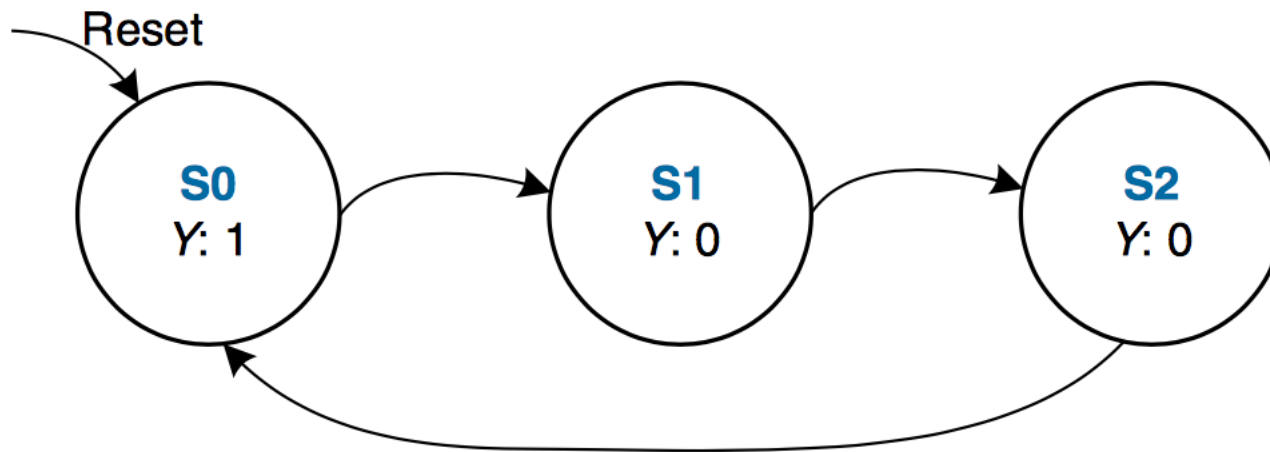The output **Y** is HIGH for **one clock cycle out of every 3**. In other words, the output **divides the frequency of the clock by 3**.




Implementing FSM Example 1: Definitions

```
module divideby3FSM (input clk,  
                    input reset,  
                    output y);  
  
    reg [1:0] state, nextstate;  
  
    parameter S0 = 2'b00;  
    parameter S1 = 2'b01;  
    parameter S2 = 2'b10;
```

- We define `state` and `nextstate` as 2-bit reg
- The parameter descriptions are `optional`, it makes reading easier


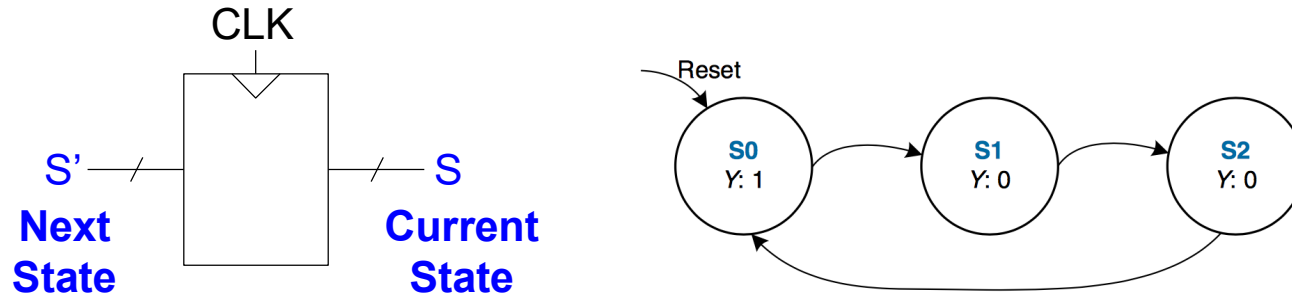
Implementing FSM Example 1: State Register



```
// state register
always @ (posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;
```



- This part defines the **state register** (memorizing process)
- Sensitive to only **clk**, **reset**
- In this example, **reset** is active when it is '1' (active-high)

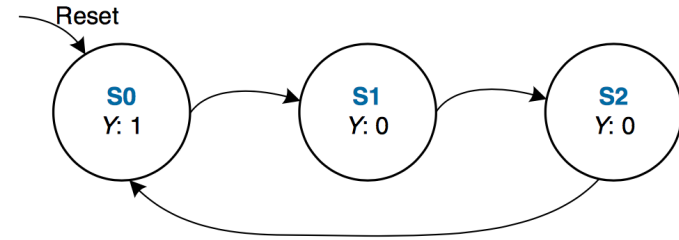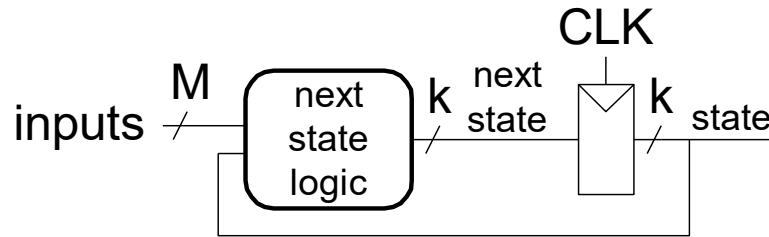Implementing FSM Example 1: Next State Logic



```
// next state logic
always @ (*)
  case (state)
    S0:    nextstate = S1;
    S1:    nextstate = S2;
    S2:    nextstate = S0;
    default: nextstate = S0;
  endcase
```


Implementing FSM Example 1: Output Logic

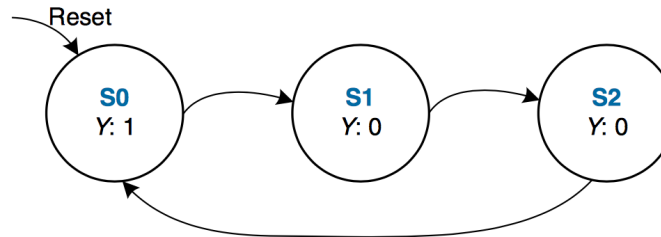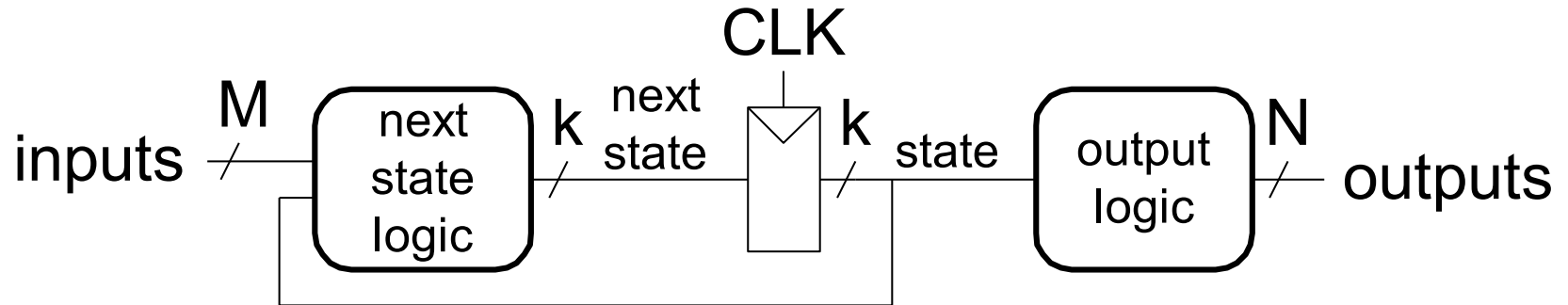

```
// output logic
assign y = (state == S0);
```

- In this example, output depends only on state
 - **Moore type FSM**

Full Implementation of FSM Example 1

```
module divideby3FSM (input clk, input reset, output y);
    reg [1:0] state, nextstate;

    parameter S0 = 2'b00; parameter S1 = 2'b01; parameter S2 = 2'b10;


    always @ (posedge clk, posedge reset) // state register
        if (reset) state <= S0;
        else      state <= nextstate;

    always @ (*) // next state logic
        case (state)
            S0:      nextstate = S1;
            S1:      nextstate = S2;
            S2:      nextstate = S0;
            default: nextstate = S0;
        endcase


    assign y = (state == S0); // output logic
endmodule
```

FSM Example 2: Recall the Smiling Snail

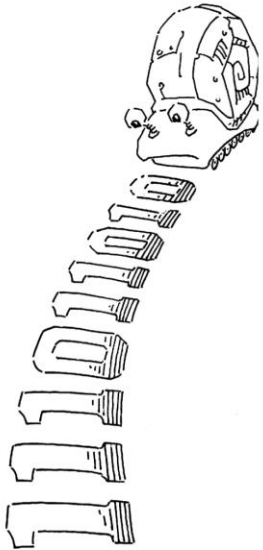
- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it
- The snail smiles whenever the last four digits it has crawled over are **1101**
- Design Moore and Mealy FSMs of the snail's brain



Moore

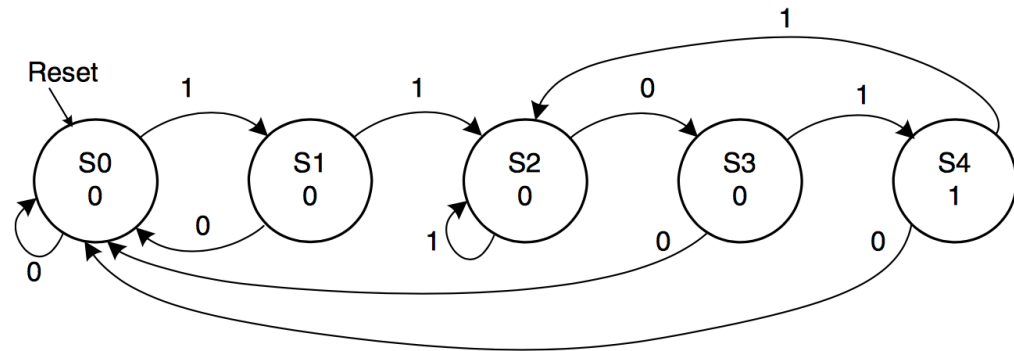


Mealy

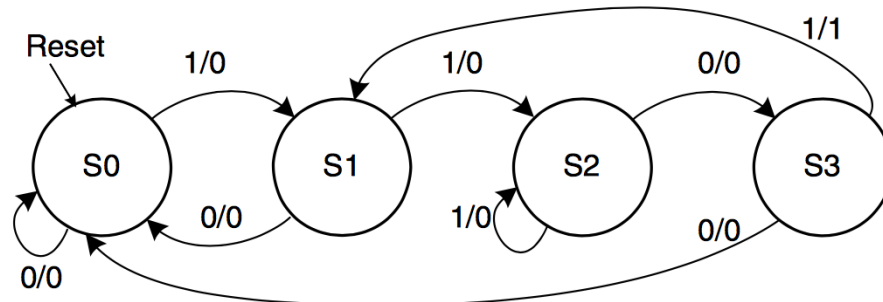

Implementing FSM Example 2: Definitions
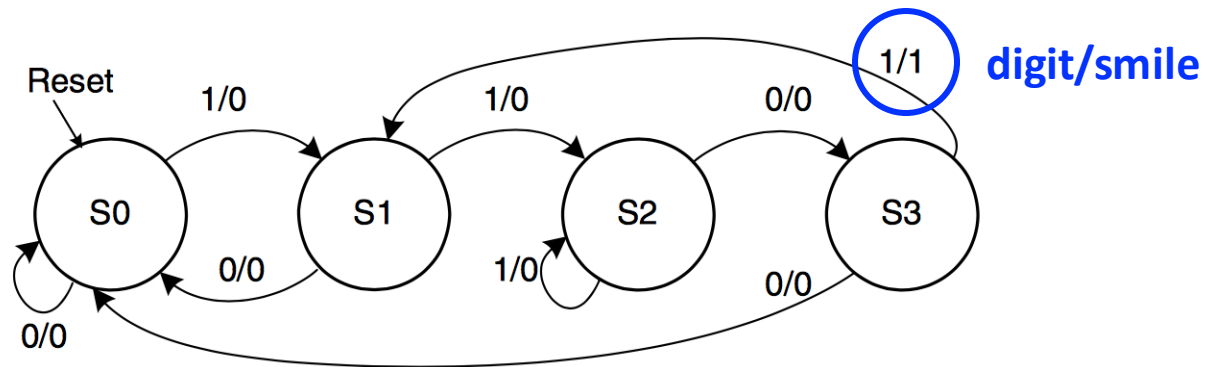
```
module SmilingSnail (input clk,  
                    input reset,  
                    input digit,  
                    output smile);  
  
    reg [1:0] state, nextstate;  
  
    parameter S0 = 2'b00;  
    parameter S1 = 2'b01;  
    parameter S2 = 2'b10;  
    parameter S3 = 2'b11;
```




Implementing FSM Example 2: State Register

```
// state register
always @ (posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;
```

- This part defines the **state register** (memorizing process)
- Sensitive to only **clk**, **reset**
- In this example **reset** is active when '1' (active-high)

Implementing FSM Example 2: Next State Logic
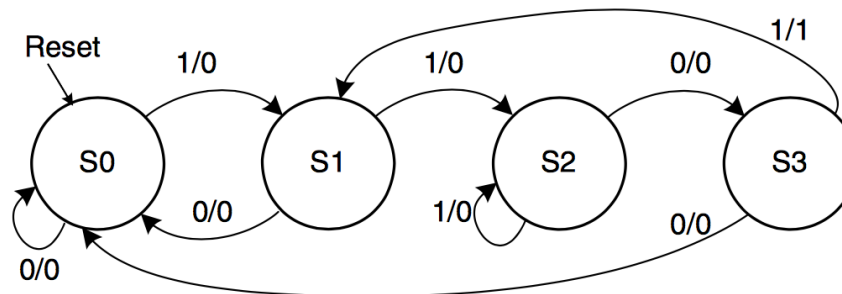
```
// next state logic
always @ (*)
  case (state)
    S0: if (digit) nextstate = S1;
        else nextstate = S0;
    S1: if (digit) nextstate = S2;
        else nextstate = S0;
    S2: if (digit) nextstate = S2;
        else nextstate = S3;
    S3: if (digit) nextstate = S1;
        else nextstate = S0;
    default: nextstate = S0;
  endcase
```



Implementing FSM Example 2: Output Logic

```
// output logic  
assign smile = (digit & state == S3);
```

- In this example, output depends on state and input
 - **Mealy type FSM**
- We used a simple combinational assignment

Implementation of FSM Example 2

```
module SmilingSnail (input clk,
                    input reset,
                    input digit,
                    output smile);

    reg [1:0] state, nextstate;

    parameter S0 = 2'b00;
    parameter S1 = 2'b01;
    parameter S2 = 2'b10;
    parameter S3 = 2'b11;

    // state register
    always @ (posedge clk, posedge
reset)
        if (reset) state <= S0;
        else      state <= nextstate;
```

```
    always @ (*) // next state logic
        case (state)
            S0: if (digit)
                    nextstate = S1;
                else nextstate = S0;
            S1: if (digit)
                    nextstate = S2;
                else nextstate = S0;
            S2: if (digit)
                    nextstate = S2;
                else nextstate = S3;
            S3: if (digit)
                    nextstate = S1;
                else nextstate = S0;
            default: nextstate = S0;
        endcase
    // output logic
    assign smile = (digit & state==S3);

endmodule
```


What Did We Learn?

- Basics of describing **sequential circuits** in Verilog
- The **always** statement
 - ❑ Needed for describing memorizing elements (**flip-flops, latches**)
 - ❑ Can also be used to describe **combinational circuits**
- **Blocking** vs **Non-blocking** statements
 - ❑ **=** assigns the value **immediately**
 - ❑ **<=** assigns the value **at the end of the block**
- **Describing FSMs in Verilog**
 - ❑ Next state logic
 - ❑ State assignment
 - ❑ Output logic

Digital Design & Computer Arch.

Lecture 5: Hardware Description Languages and Verilog

Prof. Onur Mutlu

ETH Zürich


Spring 2026

5 March 2026

Finite State Machine: State Encoding

FSM State Encoding

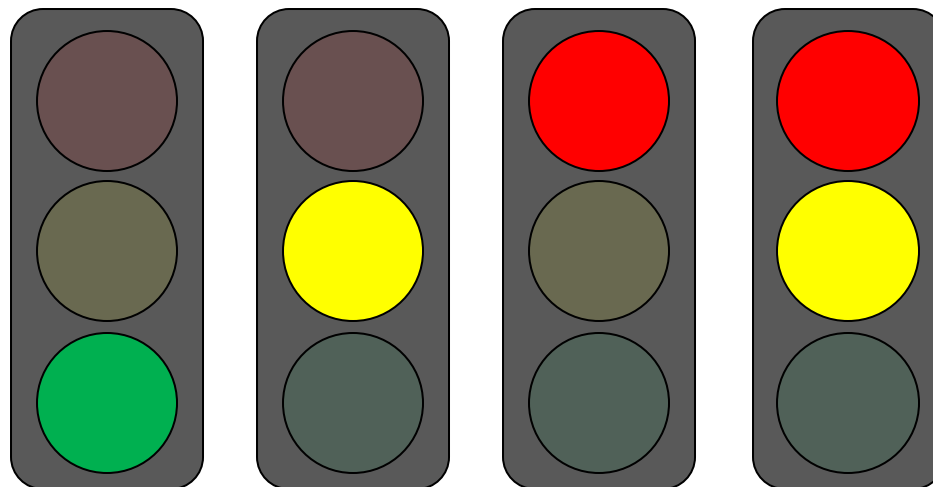- How do we encode the state bits?
 - Three common state binary encodings with different tradeoffs
 1. **Fully Encoded**
 2. **1-Hot Encoded**
 3. **Output Encoded**
- Let's see an example **Swiss** traffic light with 4 states
 - Green, Yellow, Red, Yellow+Red



FSM State Encoding (II)

1. Binary Encoding (Full Encoding):

- ❑ Use the minimum possible number of bits
 - Use $\log_2(num_states)$ bits to represent the states
- ❑ *Example state encodings: 00, 01, 10, 11*
- ❑ **Minimizes** # flip-flops, but not necessarily output logic or next state logic

2. One-Hot Encoding:

- ❑ Each bit encodes a different state
 - Uses num_states bits to represent the states
 - Exactly 1 bit is “hot” for a given state
- ❑ *Example state encodings: 0001, 0010, 0100, 1000*
- ❑ **Simplest design process** – very automatable
- ❑ **Minimizes** next state logic, **maximizes** # flip-flops

FSM State Encoding (III)

3. Output Encoding:

- ❑ Outputs are **directly accessible** in the state encoding
- ❑ For example, since we have **3 outputs** (light color), encode state with **3 bits**, where each bit represents a color
- ❑ *Example states:* 001, 010, 100, 110
 - Bit₀ encodes **green** light output,
 - Bit₁ encodes **yellow** light output
 - Bit₂ encodes **red** light output
- ❑ **Minimizes** output logic
- ❑ Only works for Moore Machines (output function of state)

FSM State Encoding (III)

3. Output Encoding:

- Outputs are **directly accessible** in the state encoding

The **designer** must **carefully** choose an encoding scheme to **optimize** the design under given constraints


- **Minimizes** output logic
- Only works for Moore Machines (output depends only on state)

Moore vs. Mealy Machines


Recall: Moore vs. Mealy FSMs

- Next state is determined by the current state and the inputs
- Two types of FSMs differ in the **output logic**:
 - **Moore FSM**: outputs depend only on the current state
 - **Mealy FSM**: outputs depend on the current state and the inputs

Moore FSM

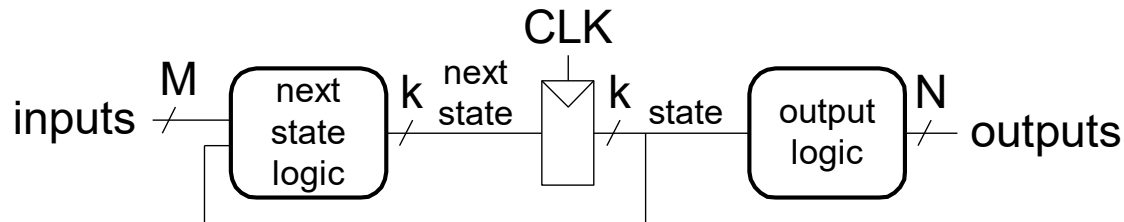


Mealy FSM

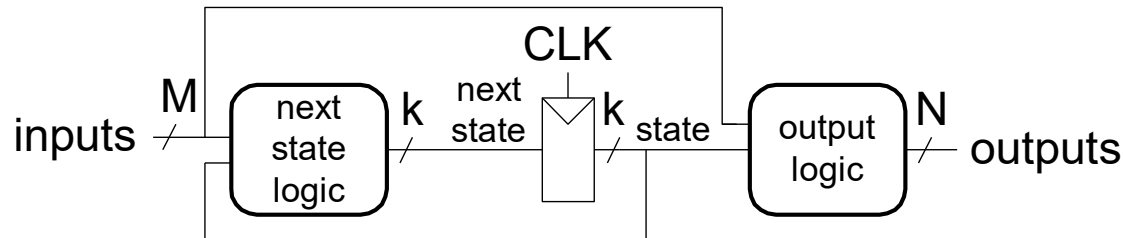



Moore vs. Mealy FSM Examples

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.

Moore FSM

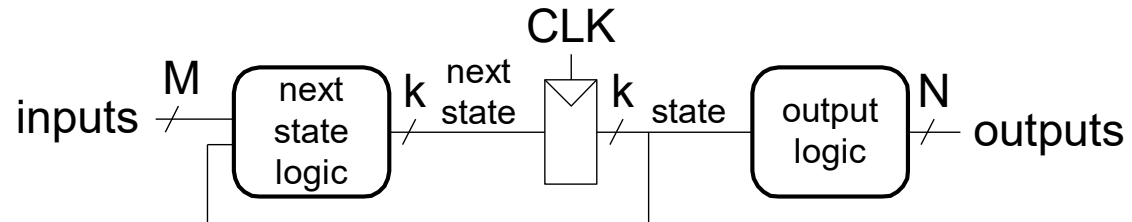


Mealy FSM

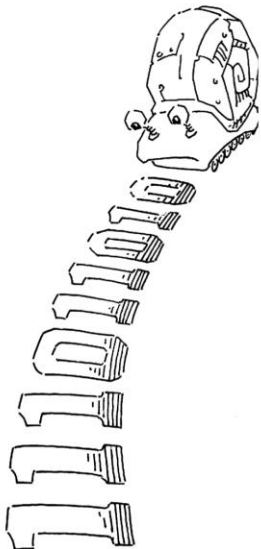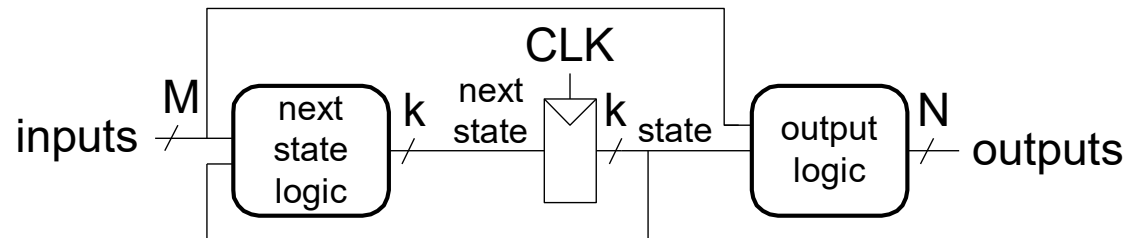



Moore vs. Mealy FSM Examples

- Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it.
- The snail smiles whenever the last four digits it has crawled over are **1101**.
- Design Moore and Mealy FSMs of the snail's brain.

Moore FSM

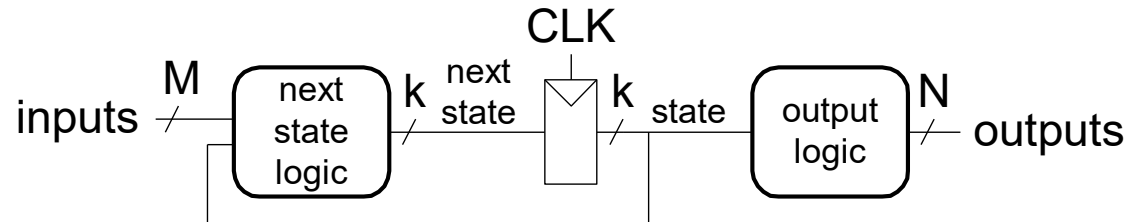


Mealy FSM

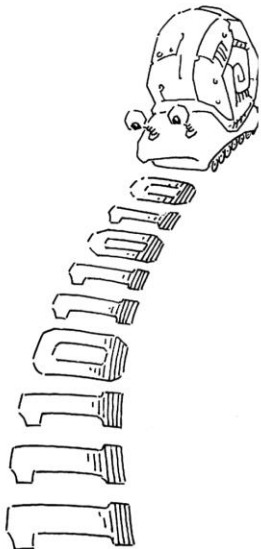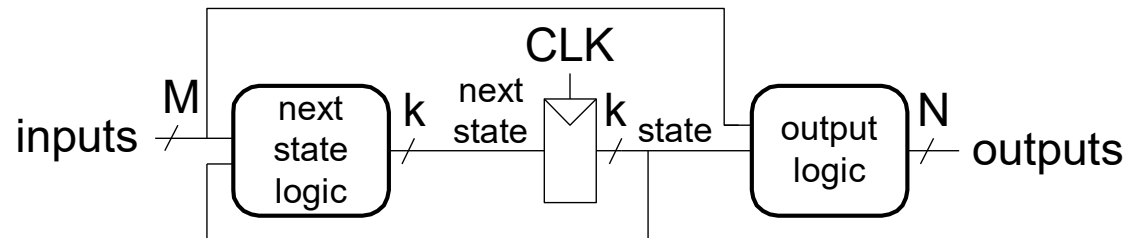



State Transition Diagrams

Moore FSM

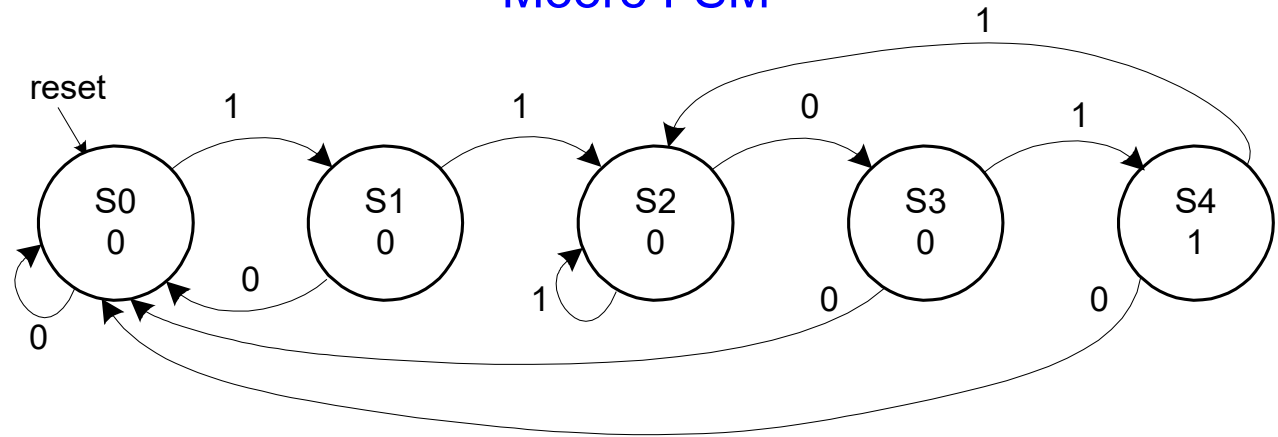

What are the tradeoffs?

Mealy FSM

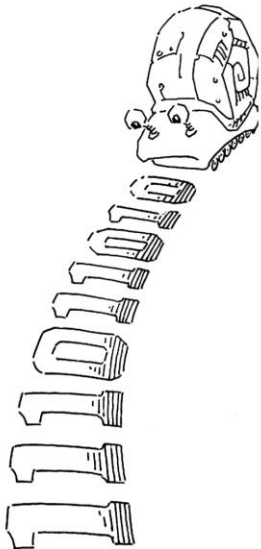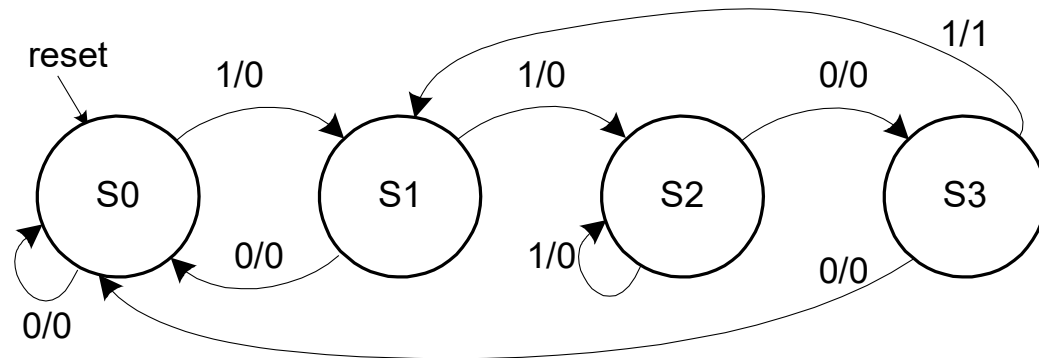

FSM Design Procedure

- **Determine** all possible states of your machine
- **Develop** a **state transition diagram**
 - Generally this is done from a textual description
 - You need to 1) determine the **inputs** and **outputs** for each **state** and 2) figure out how to get from one state to another
- **Approach**
 - Start by defining the **reset state** and what happens from it – this is typically an easy point to start from
 - Then continue to add **transitions** and **states**
 - Picking **good state names** is very important
 - Building an FSM is **like** programming (but it *is not* programming!)
 - An FSM has a sequential “control-flow” like a program with conditionals and goto’s
 - The if-then-else construct is controlled by one or more inputs
 - The outputs are controlled by the state or the inputs
 - In hardware, we typically have many concurrent FSMs

What is to Come: LC-3 Processor



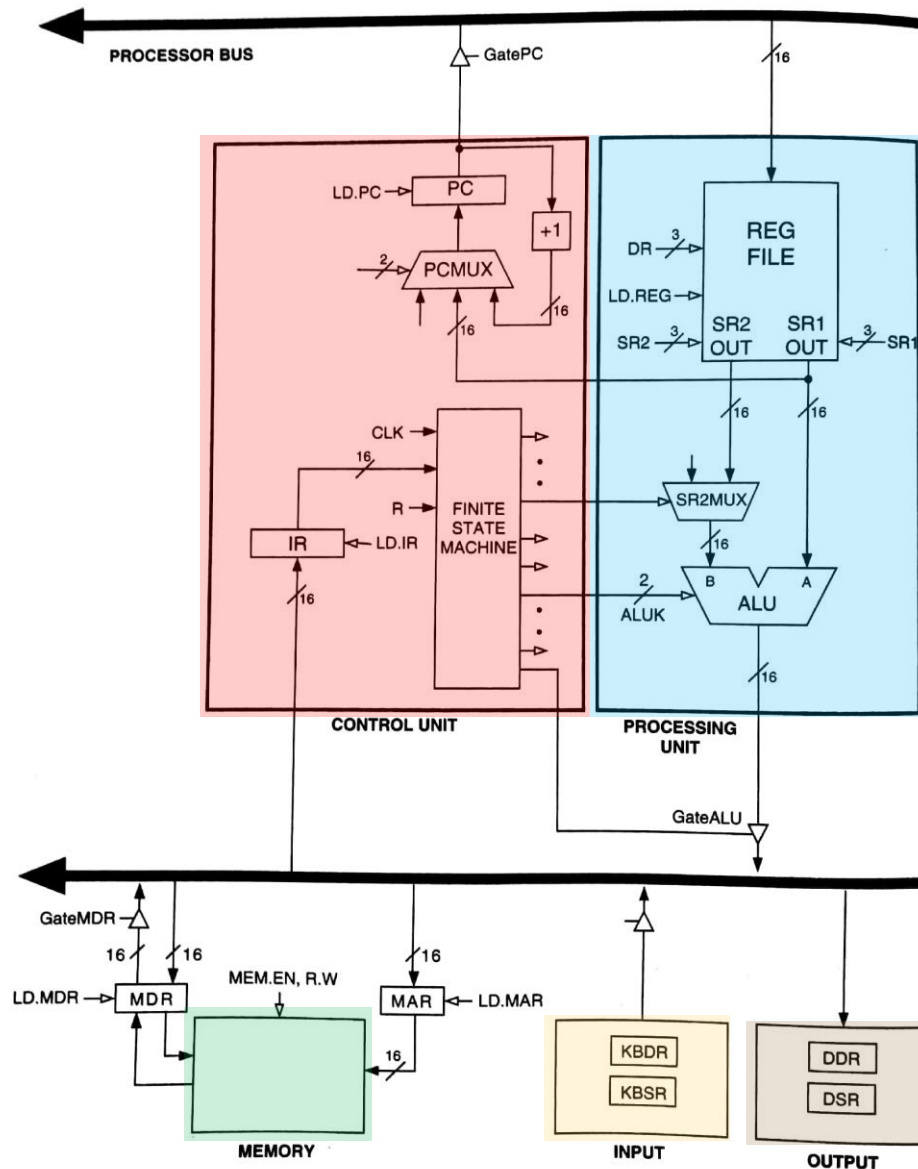


Figure 4.3 The LC-3 as an example of the von Neumann model

What is to Come: LC-3 Datapath

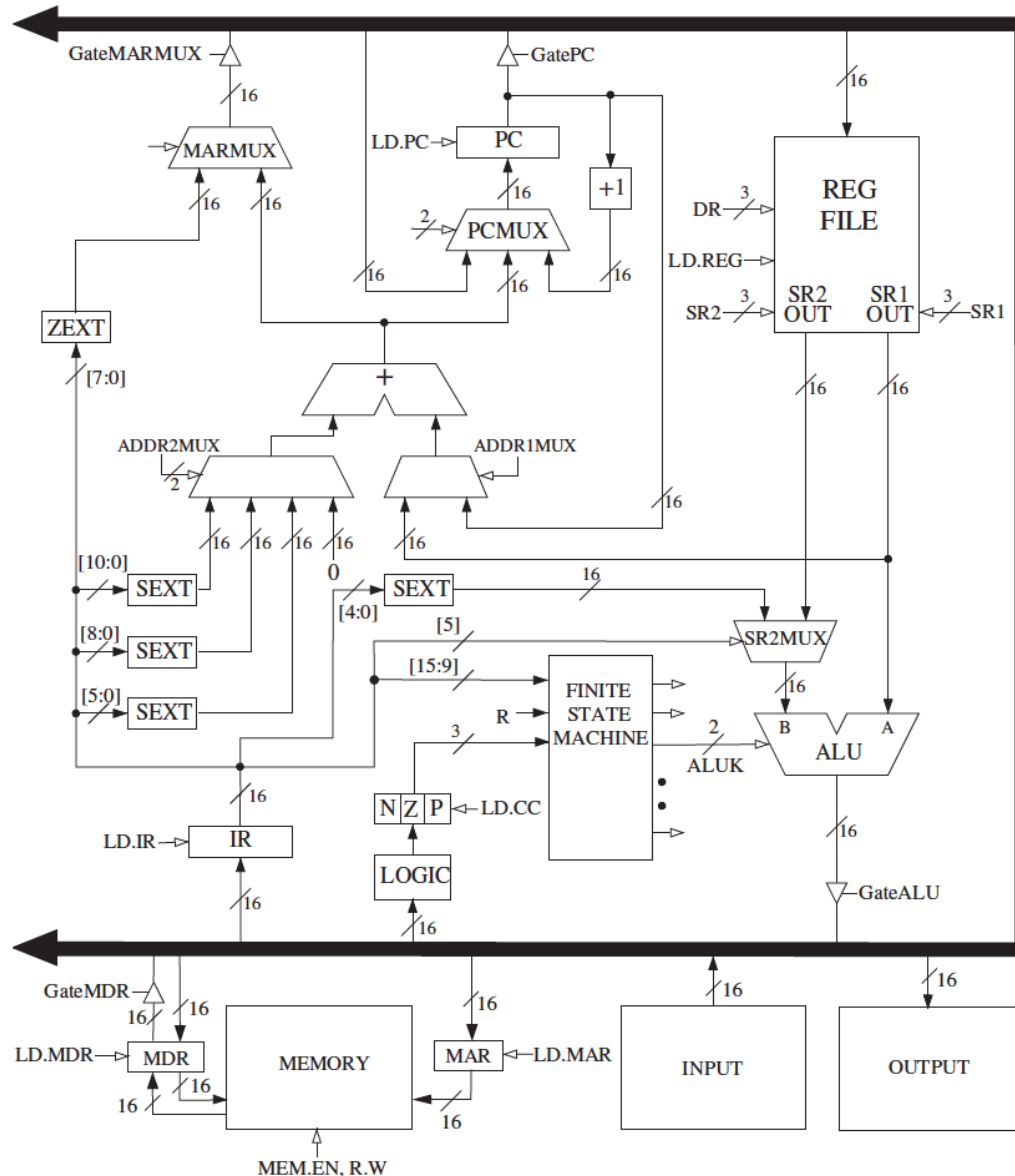

Recall: Synchronous Sequential Circuits

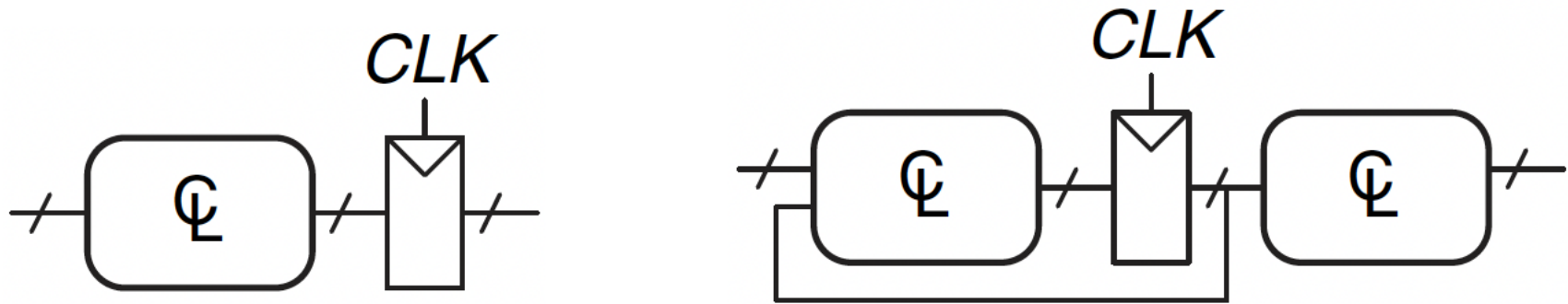

Major types of Sequential Logic Circuits

